

# High-Voltage Direct-Current Transmission Systems

Fujin Deng

School of Electrical Engineering

Southeast University

[fdeng@seu.edu.cn](mailto:fdeng@seu.edu.cn)

# Outline

---

**I. HVDC Systems**


**II. Multi-terminal HVDC Systems**

**III. DC Grid for Offshore Wind Farms**

**IV. DC-Line Fault Situations**

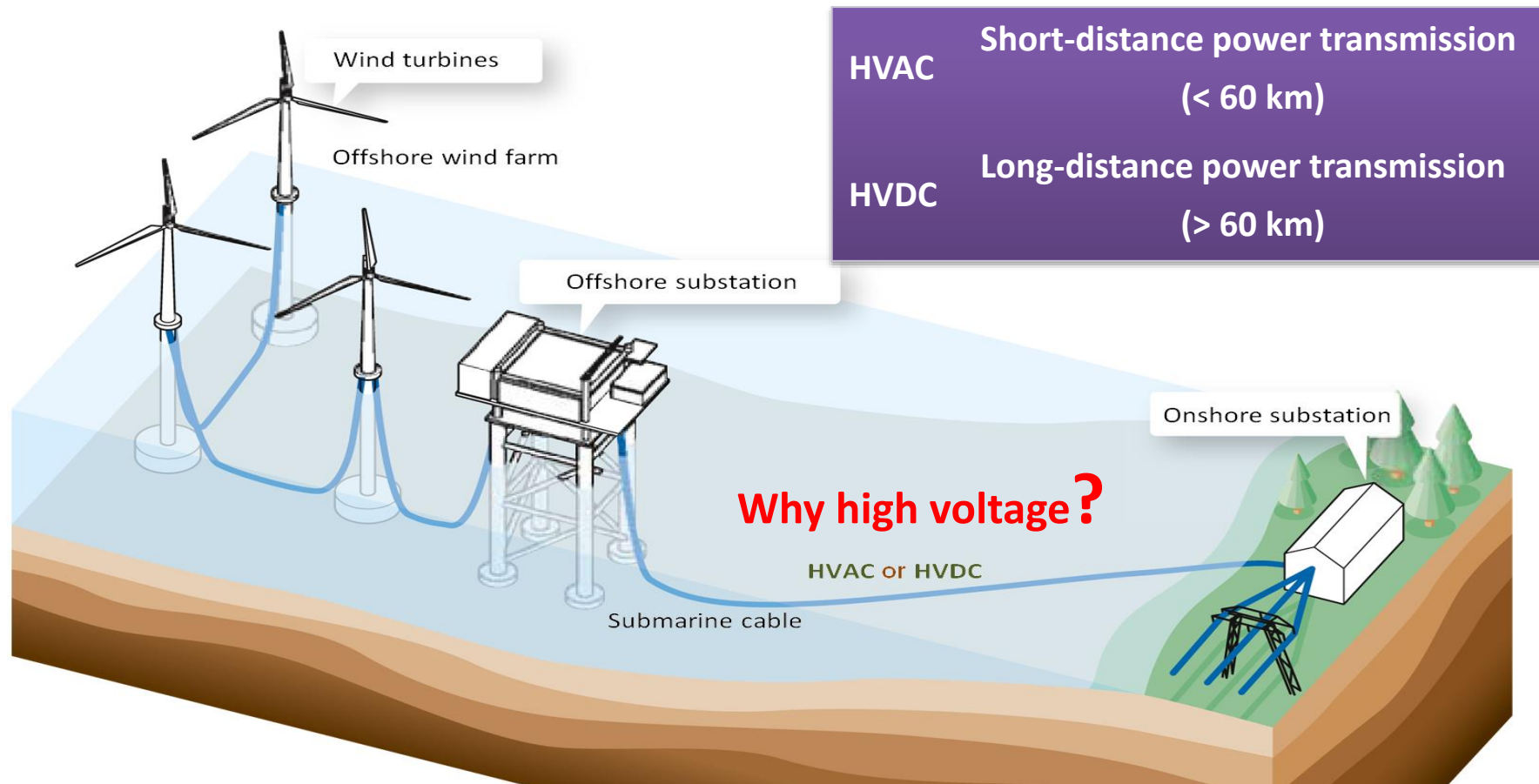
# 1 HVDC Transmission System

- ❑ High Voltage Alternative Current (HVAC) Technology
- ❑ High Voltage Direct Current (HVDC) Technology



# HVDC System Configuration
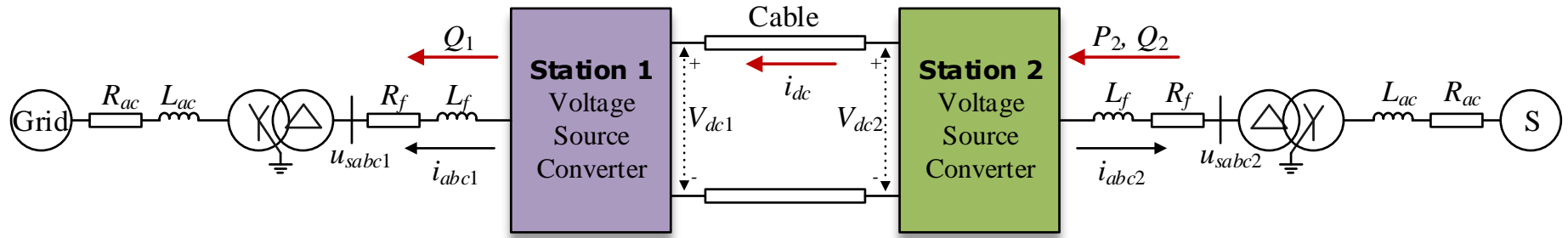
## ■ HVDC System with monopolar configuration








### ➤ Station-1

- Keep  $V_{dc1}$
- Control  $Q_1$


### ➤ Station-2

- Control  $P_2$
- Control  $Q_2$

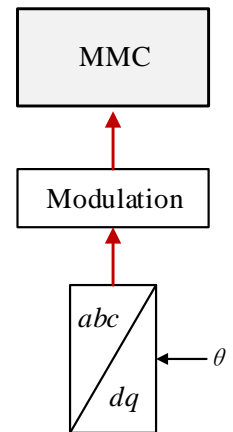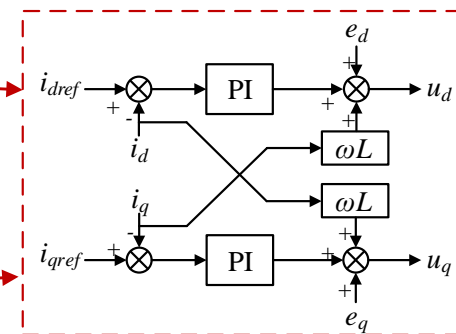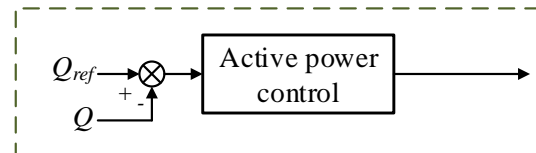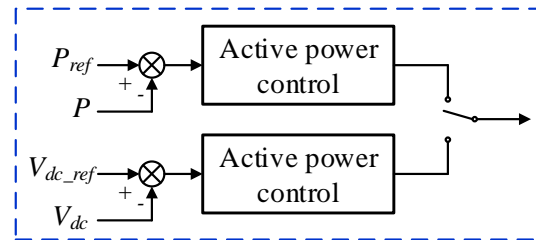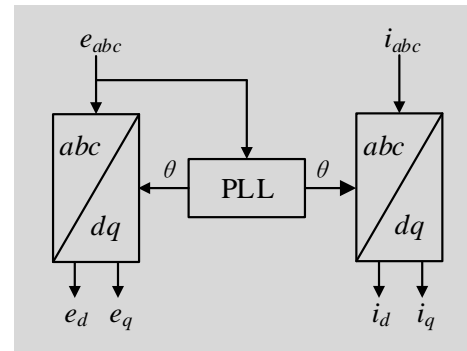


# HVDC System Configuration

## ■ Bipolar Configuration

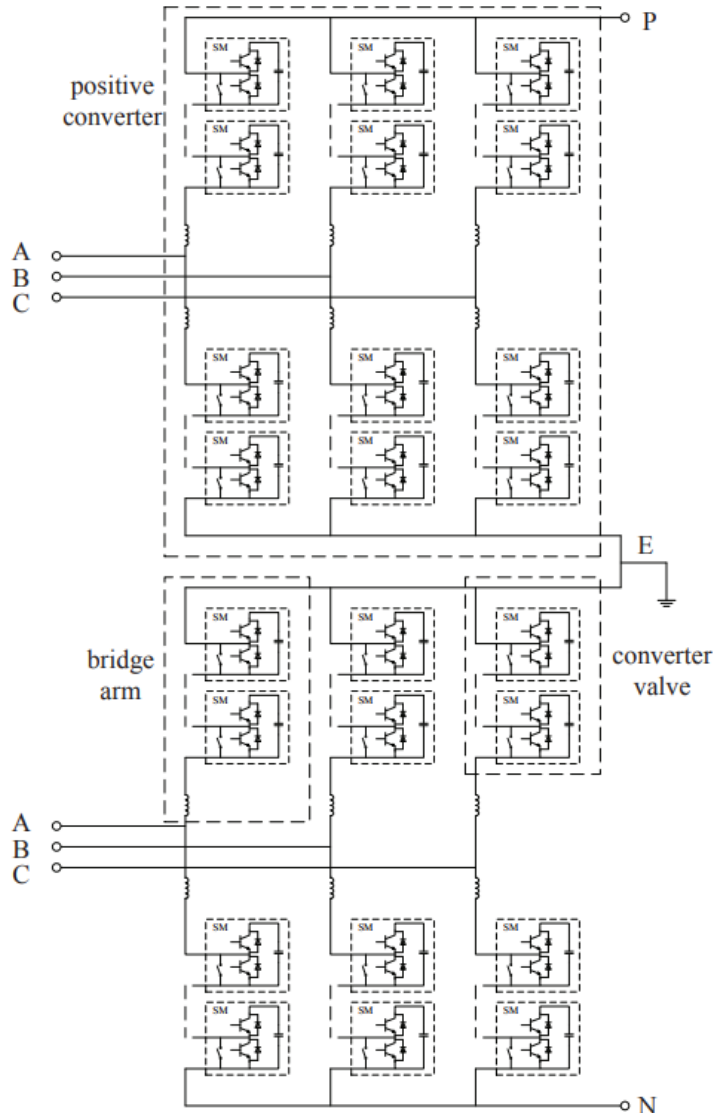


### ● Operation Mode 1

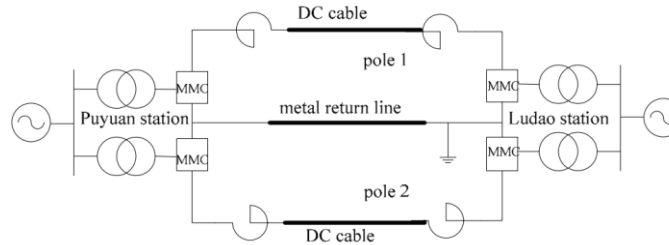


Bipolar operation  
with metal return  
line

### ● Operation Mode 2

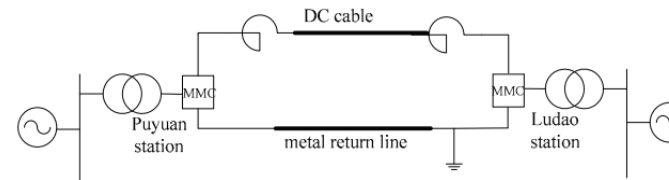


monopolar  
operation with  
metal return line

### ● Operation Mode 3

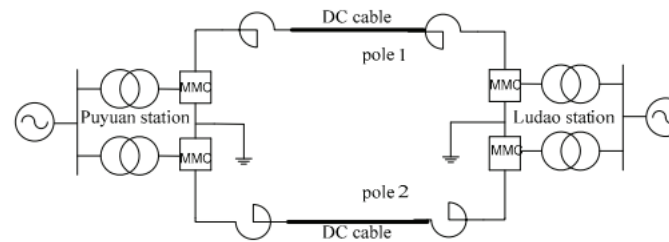

Bipolar operation  
without metal  
return line

### ● Operation Mode 4

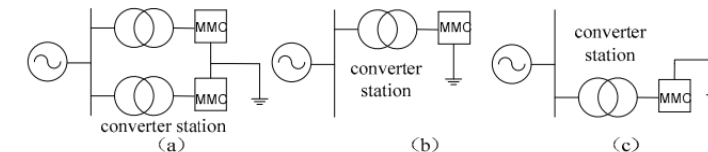

Operation as  
STATCOM

# HVDC System Configuration

## Yu-e BTB VSC-HVDC

- Com. year: 2017
- $\pm 420\text{kV}$ /1250MW, 4 channels

## Nan-Hui VSC-HVDC

- Com. Year: 2013
- $\pm 30\text{kV}$ , 18MW, 8.6km land cable

## Zhou-Shan VSC-MTDC

- Com. year: 2014
- $\pm 200\text{kV}$ , 400/300/3 $\times$ 100MW, 129 km submarine cable, 12.5 km OHL

## Luoping BTB VSC-HVDC

- Com. Year, 2016
- $\pm 350\text{kV}$ /1000MW

## Xia-Men VSC-HVDC

- Com. Year: 2015
- $\pm 320\text{kV}$ , 1000MW, 10.7 km land cable

## Guang-Dong BTB VSC-HVDC


- Com. Year: 2019
- planned

## Zhong-Hai-You VSC-HVDC

- Com. Year: 2012
- $\pm 10\text{kV}$ , 4MW, 40km submarine cable
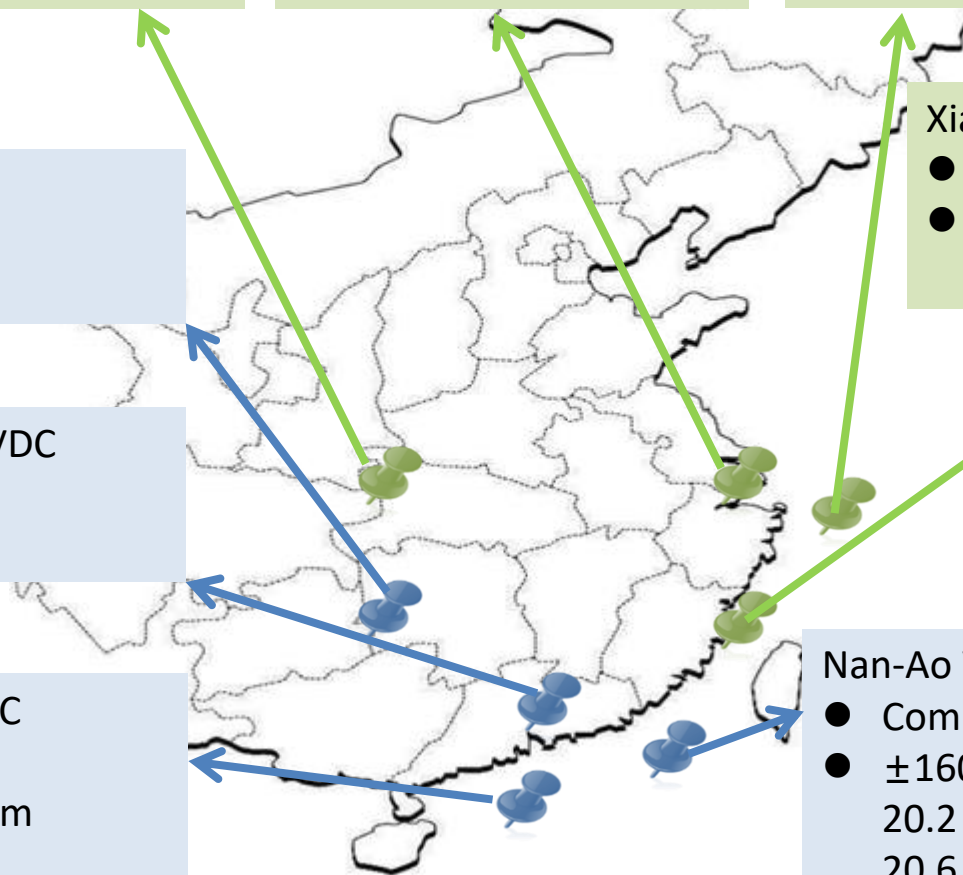
## Nan-Ao VSC-MTDC

- Com. Year: 2013
- $\pm 160\text{kV}$ , 200/100/50MW, 20.2 km land/submarine cable, 20.6 km OHL




# 2 Multi-Terminal VSC-HVDC Systems

## ■ Multi-Terminal VSC-HVDC Systems
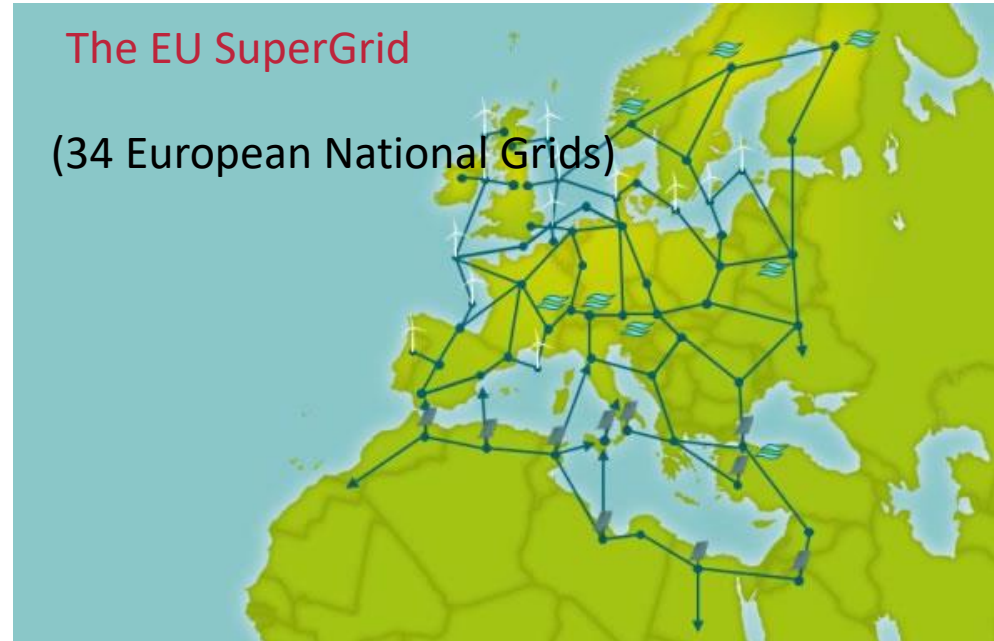
### Why VSC-MTDC ?

- Multiple power supply and multi-drop power;
- Provides additional operation flexibility,
- Redundancy
- High reliability.




### Features

- 2-Terminal System: most existing HVDC systems are point-to-point systems.
- MTDC Systems: DC transmission with 3 or more converter stations.
- For instance, the EU SuperGrid and Nan'ao VSC-MTDC project.



# Multi-Terminal VSC-HVDC Systems

## ■ Nan' ao VSC-MTDC project

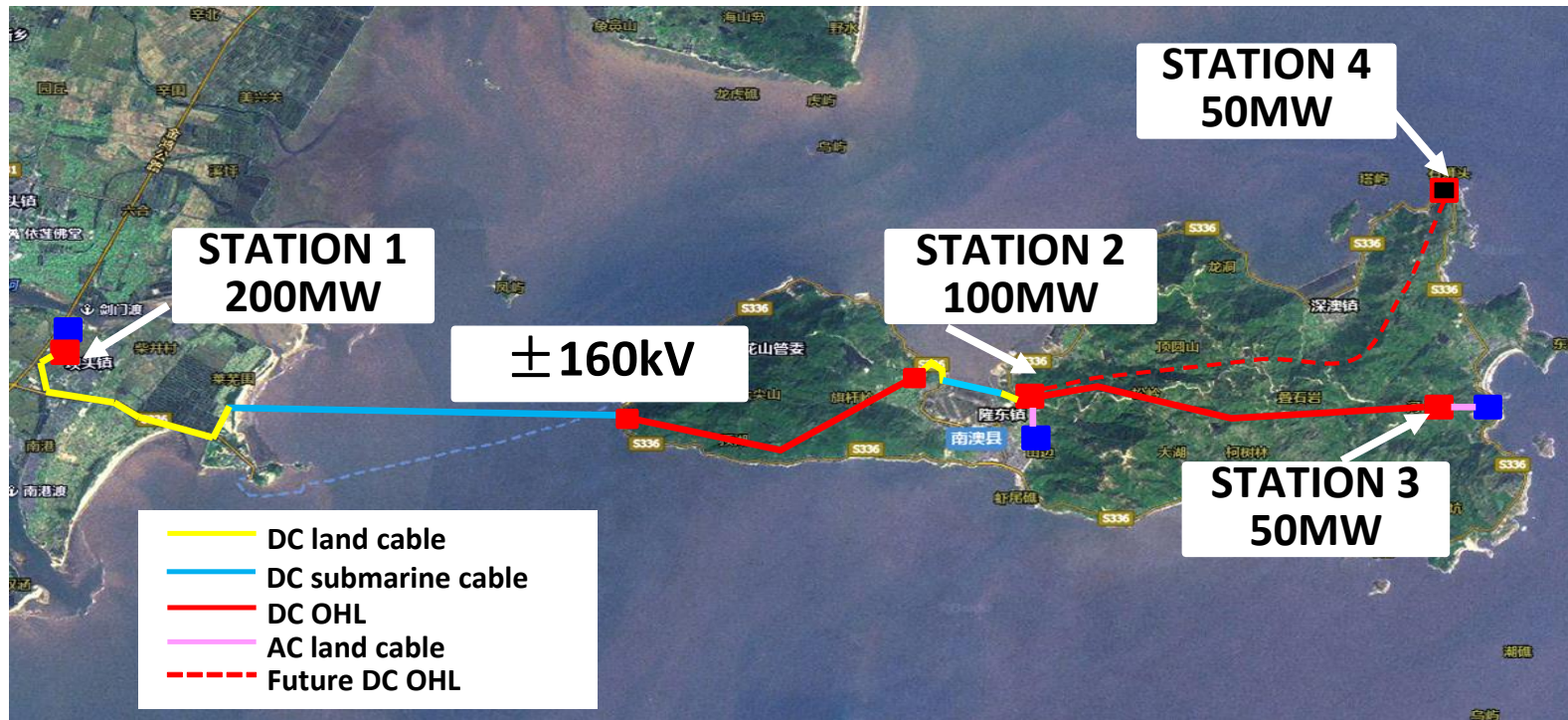

R&D  
2012-12-30

Valve test  
2013-08-01





Commissioning  
2013-10-21

Operation  
2013-12-25



# Multi-Terminal VSC-HVDC Systems


## ■ Multi-Terminal VSC-HVDC Systems Configurations

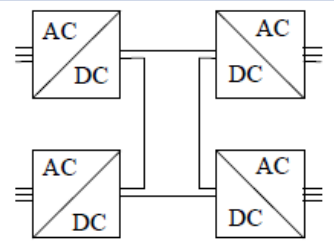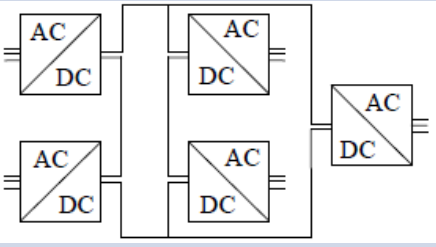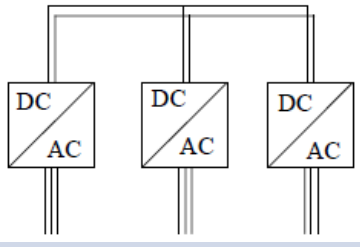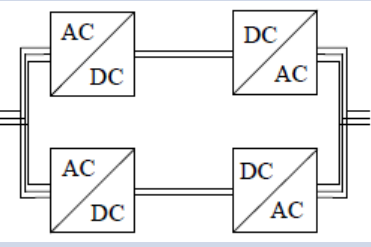	Series connection	Mixed connection	Radial parallel connection	Ring network parallel connection
Connection Topologies				
Features	<ul style="list-style-type: none"> <li>● Slow fault recovery,</li> <li>● Not conducive to the expansion of power grid because of insulation and voltage withstand requirements.</li> </ul>		<ul style="list-style-type: none"> <li>● Fast fault recovery,</li> <li>● Conducive to power grid expansion,</li> <li>● High reliability,</li> <li>● Easy maintenance,</li> <li>● Flexible operation mode.</li> </ul>	
Application	Less		Widely	

# 3 DC Grid for Offshore Wind Farm

## DC Grid

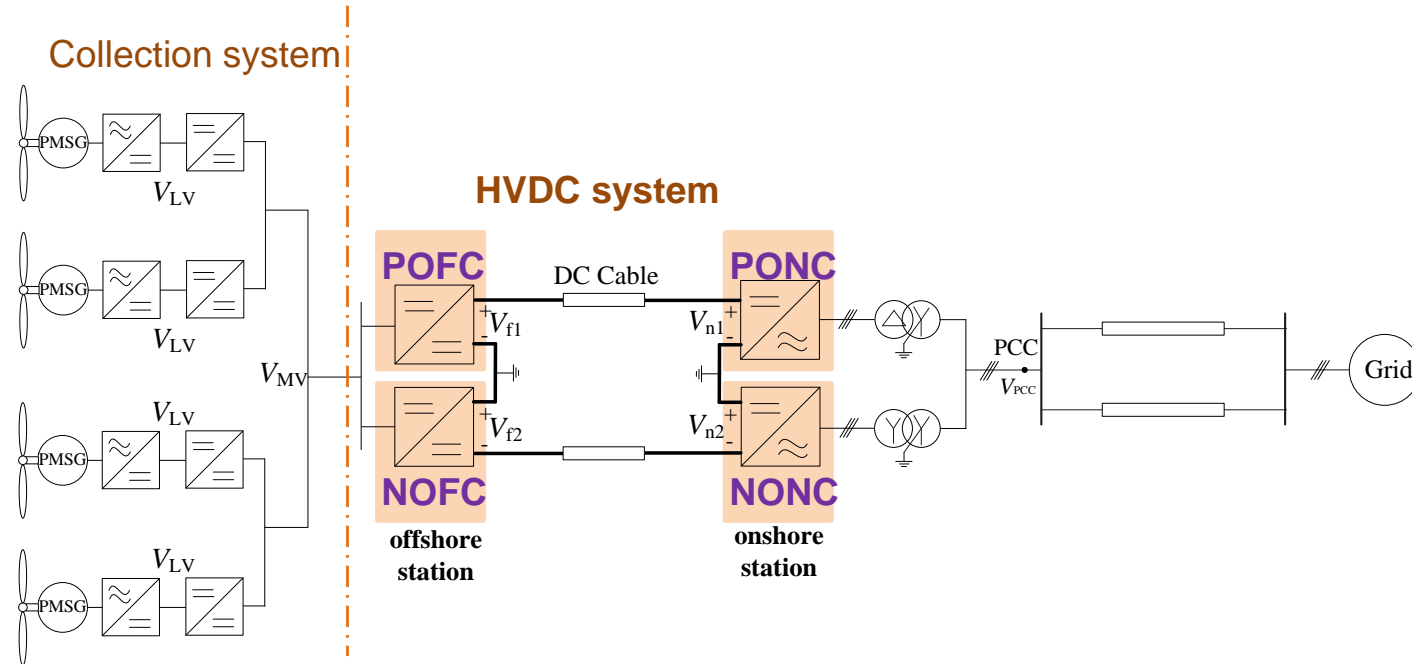
- (1) Collection system
- (2) HVDC transmission system



# Onshore Converter
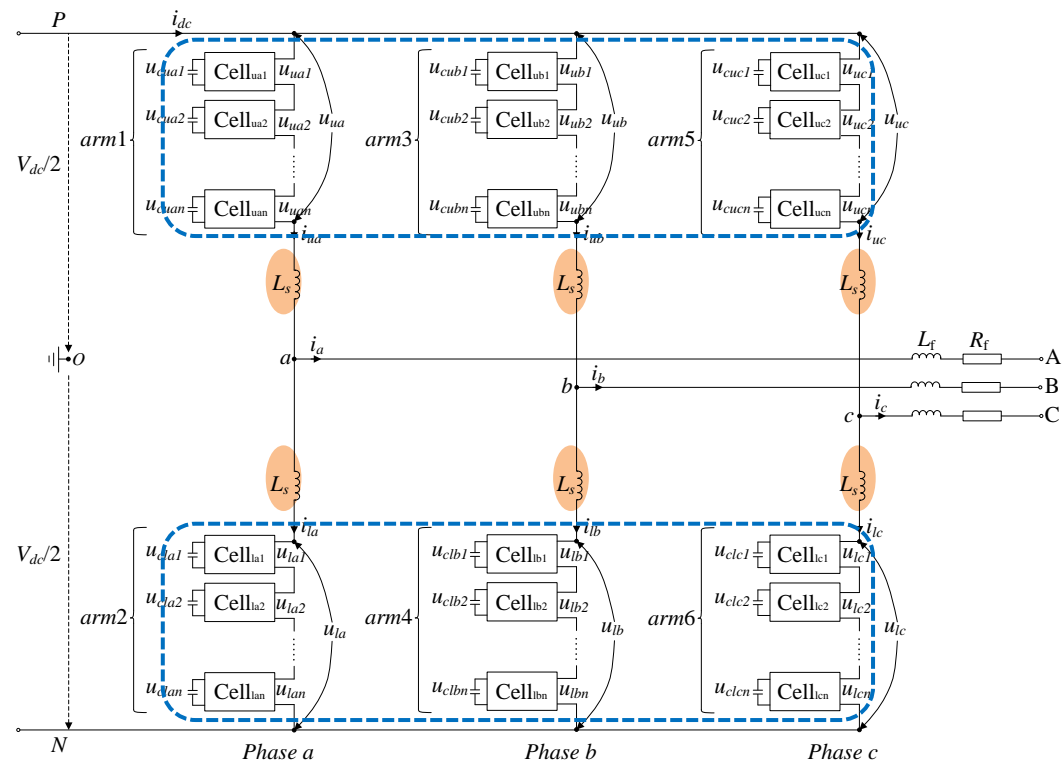
## MMC for onshore converter



- Multilevel
- Low switching frequency
- Small harmonics
- High reliability



# Onshore Converter Control
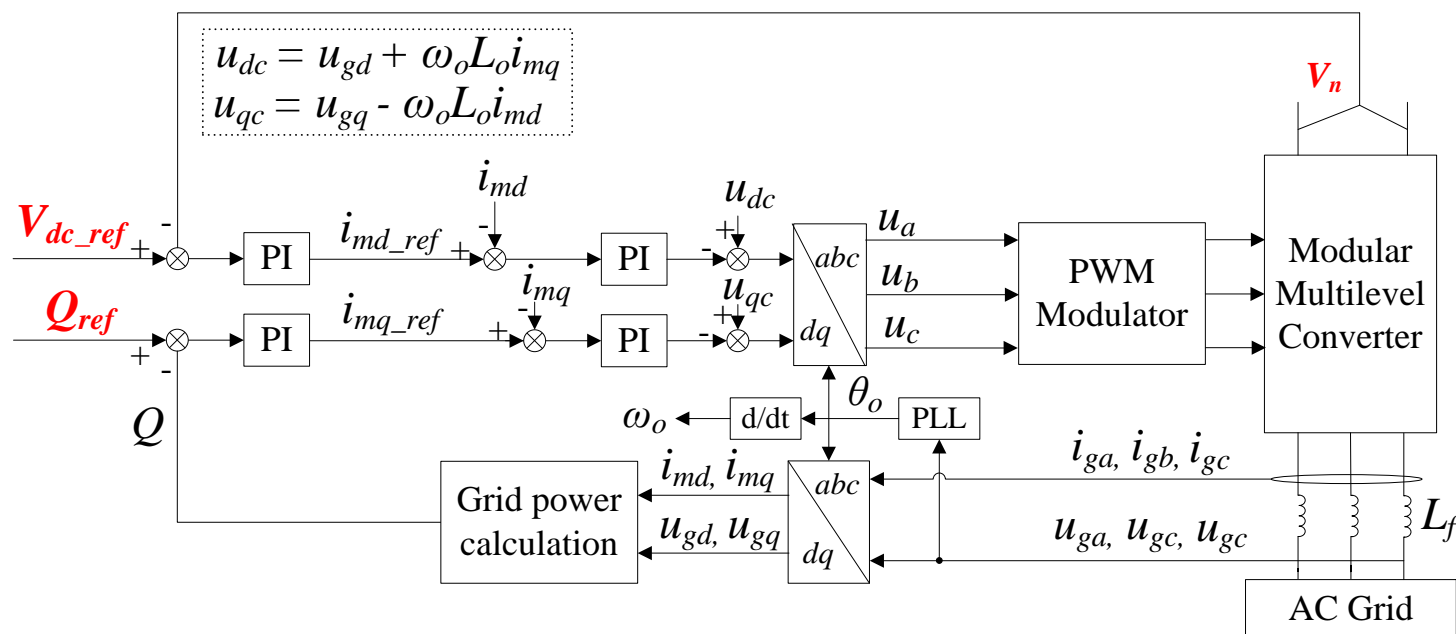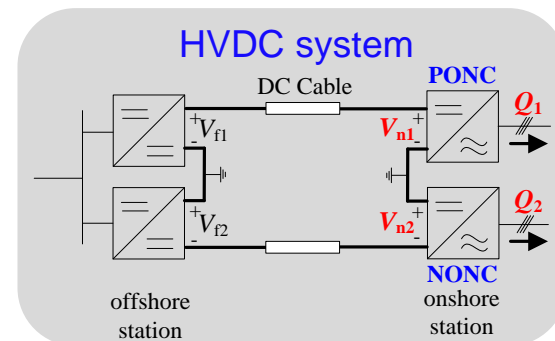
## Onshore converter (POFC & NOFC) control


- DC-link voltage control  $V_n$
- Reactive power control  $Q$



# Offshore DC/DC Converter
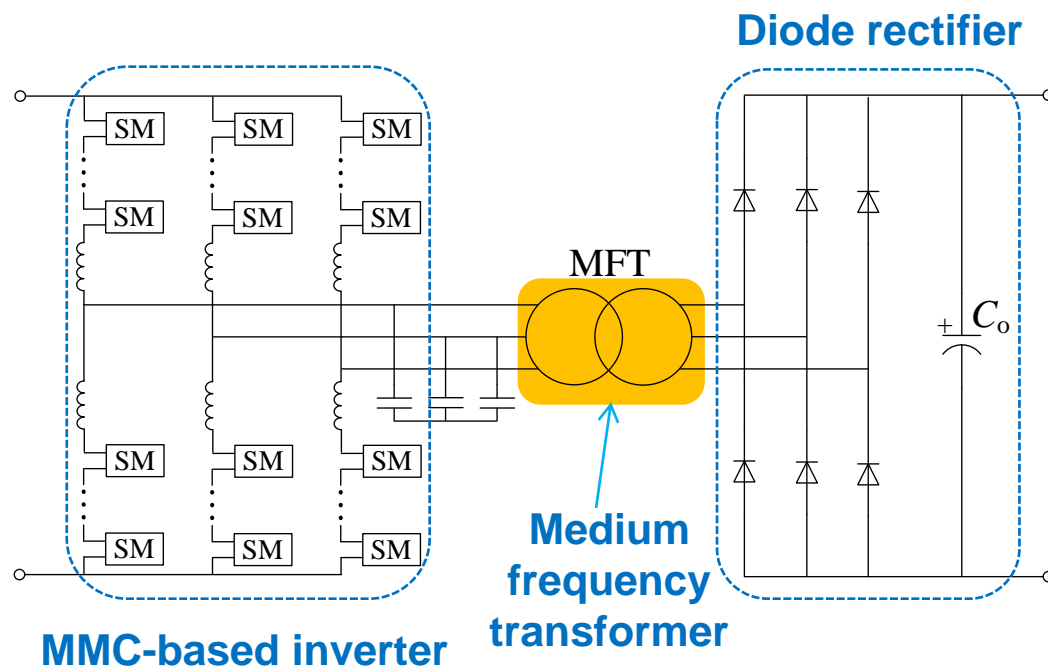
## MMC-based offshore converter



- Isolated DC transformer
- Multilevel configuration
- Medium switching frequency



# Offshore DC/DC Converter Control


## 1. Negative Offshore converter (NOFC) control

- Collection voltage control  $V_{MV}$

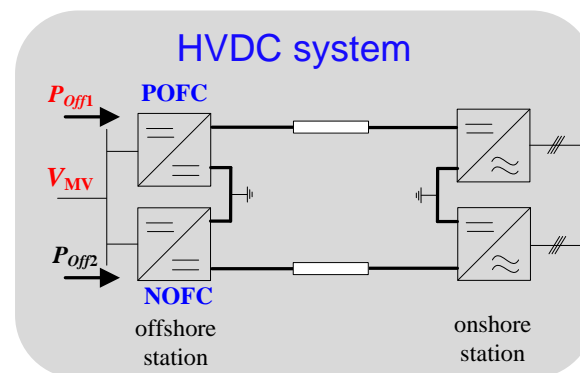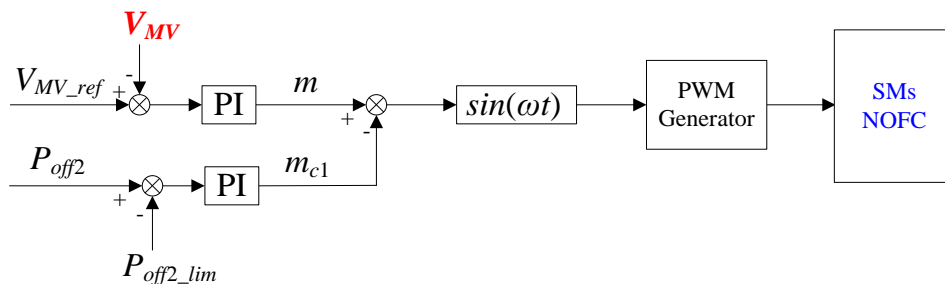

## 2. Positive Offshore converter (POFC) control


- Power follow control  $P_{off1}$

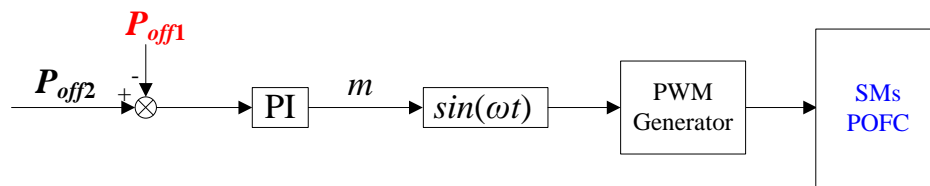

# 4 DC-Line Fault Situation

## HVDC transmission system

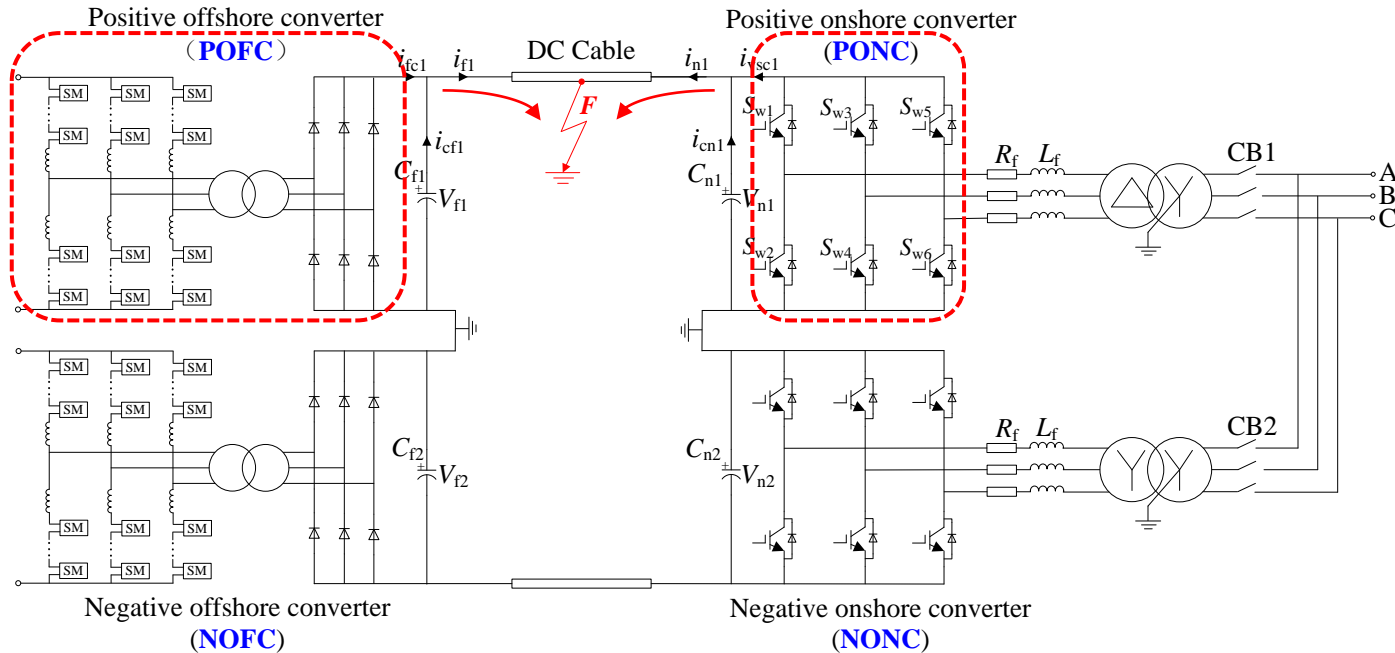- (1) Onshore converter (**PONC** & **NONC**)
- (2) Offshore converter (**POFC** & **NOFC**)






# Fault Current at Onshore Converter


## ■ Onshore converter

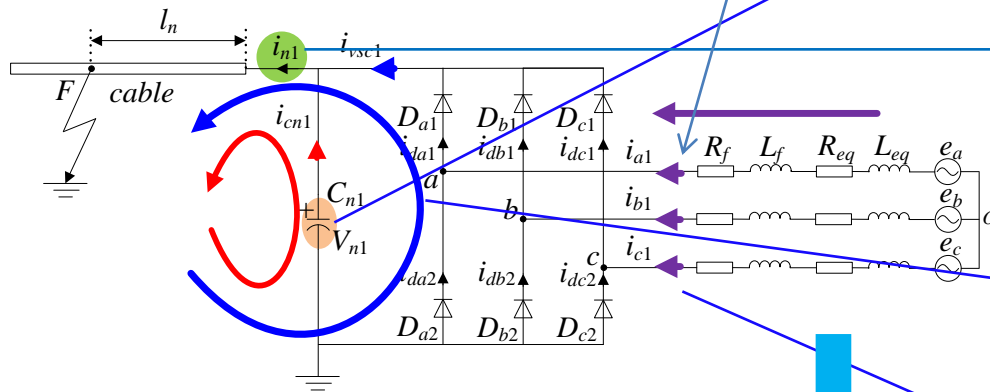- (1) Capacitor discharge
- (2) Circulating current
- (3) AC grid current


Normal operation  
 $I_m = 2.1 \text{ kA}$




$l_n = 0.1 \text{ km}$

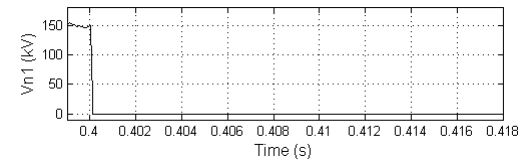


(a) Voltage  $V_{n1}$ .

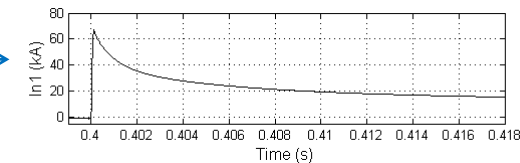

(b) Cable current  $i_{n1}$ .

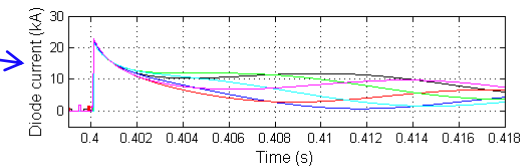


(c) Diode current.

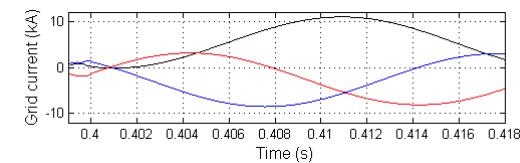


(d) Grid current.

$\text{Max}[|i_{a1}|, |i_{b1}|, |i_{c1}|]$

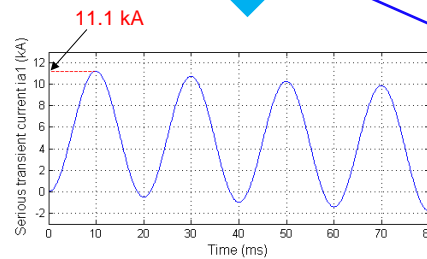

# Protective Inductor for onshore Converter
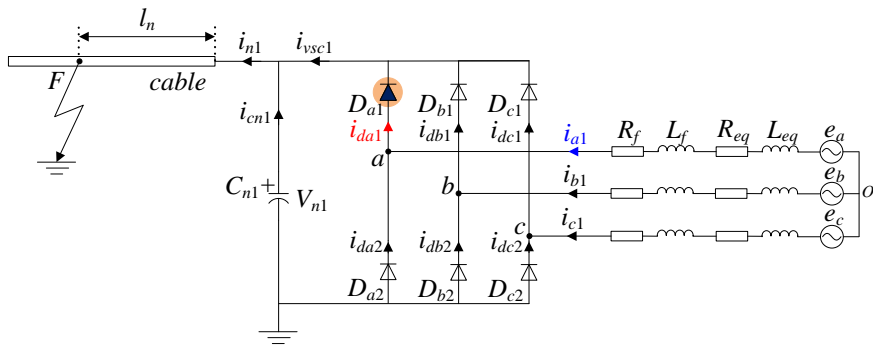
## 2. Only one diodes in one leg in condition



$$i_{dx1} = |i_{x1}|$$


$$x \in (a, b, c)$$

The possible  
maximum  
fault current

The maximum diode current is

$$i_{d2\_max} = \text{Max}[|i_{a1}|, |i_{b1}|, |i_{c1}|]$$

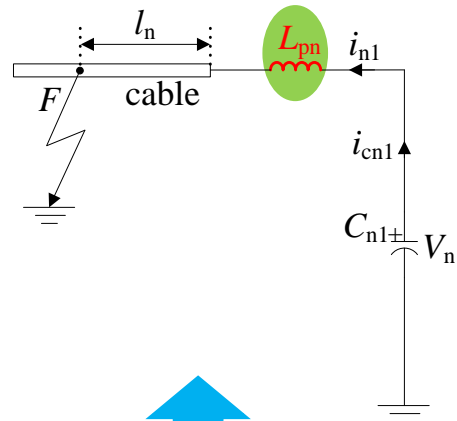
Peak value  $i_{n1m} = V_{n10} \sqrt{C_{n1}/L_{pn}}$




$$\text{Max}[i_{n1}] \leq 1.5 \text{ Max}[|i_{a1}|, |i_{b1}|, |i_{c1}|]$$

$$i_{d1\_max} \leq i_{d2\_max}$$

# Onshore Converter Performance

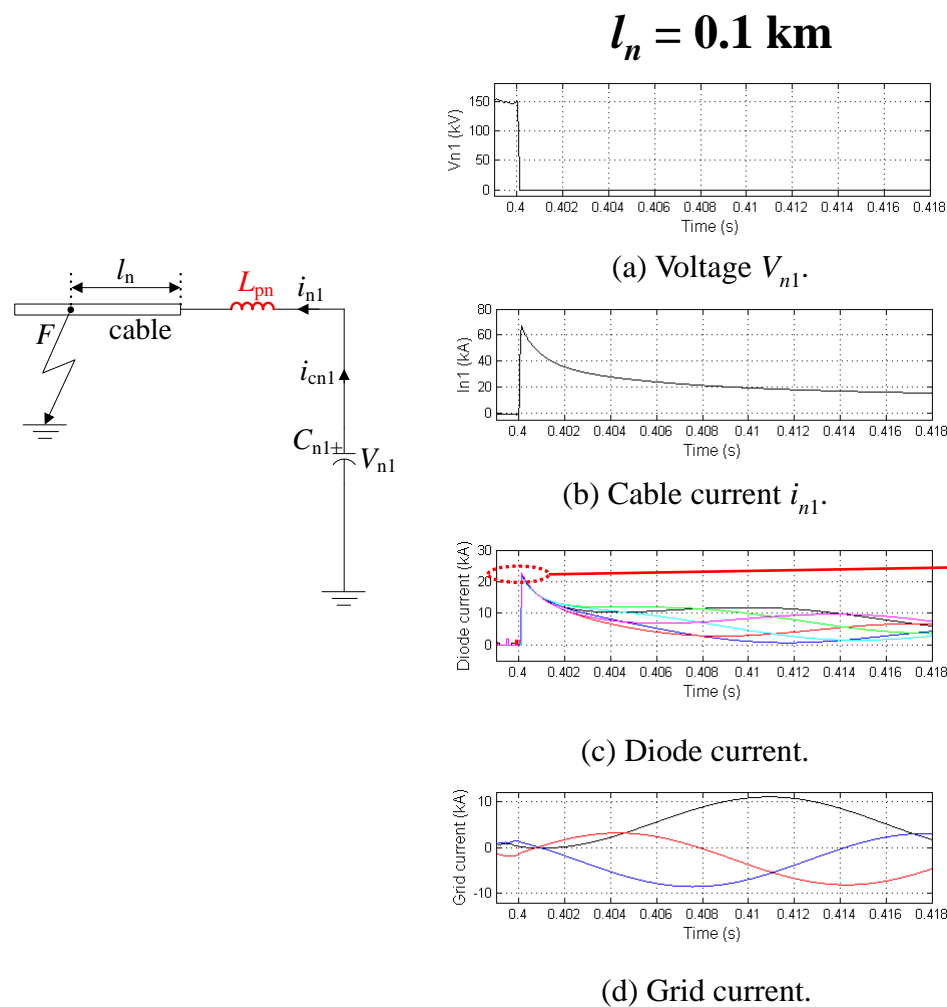

**No protection**

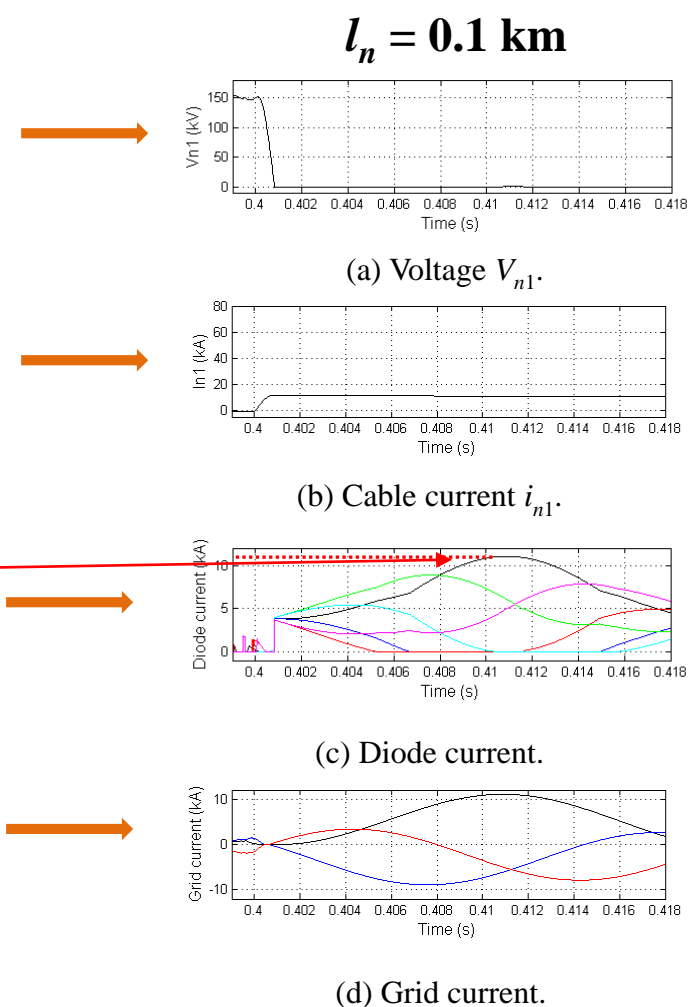


**$L_{pn}=6.5 \text{ mH}$**

# Offshore Converter Protection under Faults


## ■ Offshore converter

(1) Capacitor discharge


(2) Circulating current

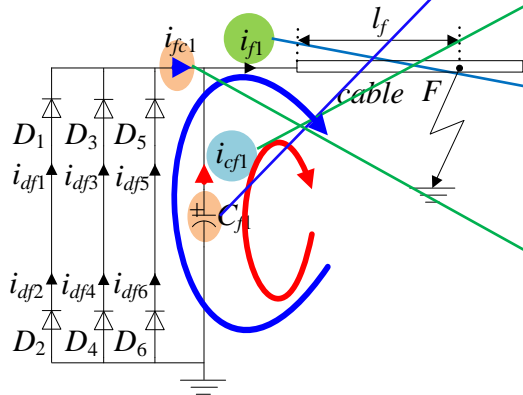


$l_n = 0.1 \text{ km}$

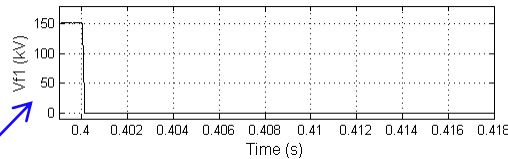


(a) Voltage  $V_{f1}$ .

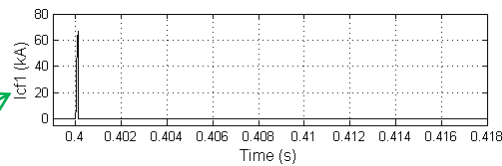

(b) Cable current  $i_{cf1}$ .

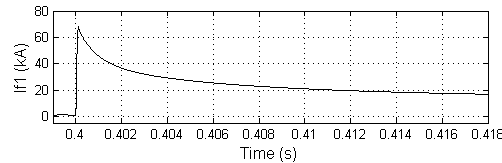


(c) Cable current  $i_{f1}$ .

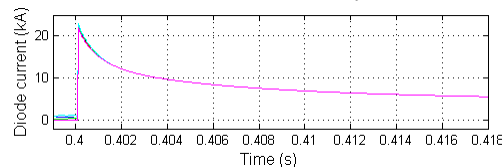

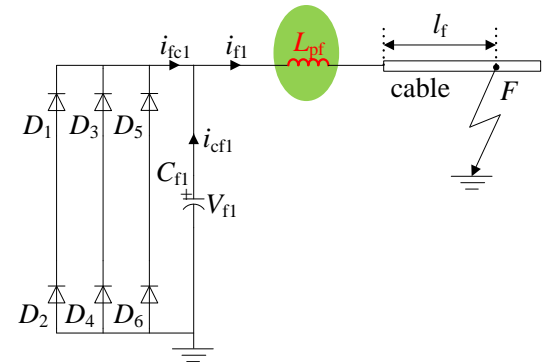
(d) Diode current.

$$\text{Peak value } i_{cf1}(t) = \sqrt{V_{f10}^2 \frac{C_{f1}}{L_{pf}} + I_{f10}^2}$$




# Offshore Converter Performance


$l_n = 0.1 \text{ km}$

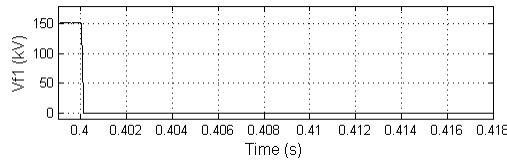


(a) Voltage  $V_{f1}$ .

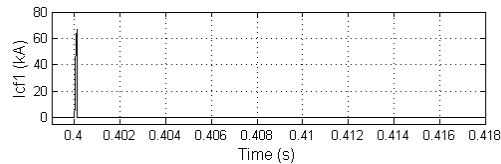

(b) Cable current  $i_{cf1}$ .

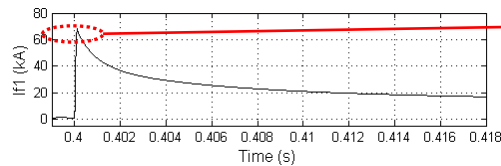


(c) Cable current  $i_{f1}$ .

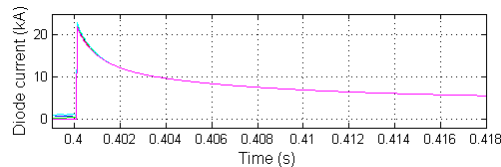


(d) Diode current.

**No protection**


$l_n = 0.1 \text{ km}$

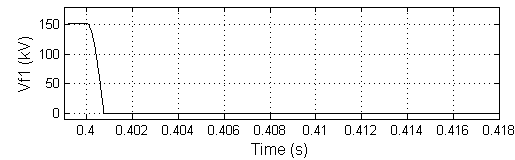


(a) Voltage  $V_{n1}$ .

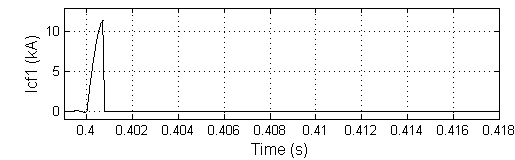

(b) Cable current  $i_{cf1}$ .

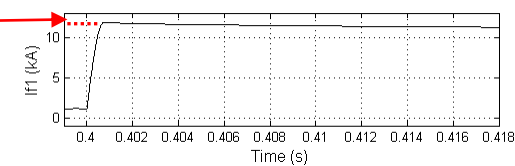

(c) Diode current.

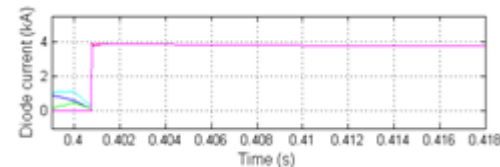


(d) Grid current.

**$L_{pf}=6.5 \text{ mH}$**

# Redundancy for HVDC System Faults

## ■ Redundancy

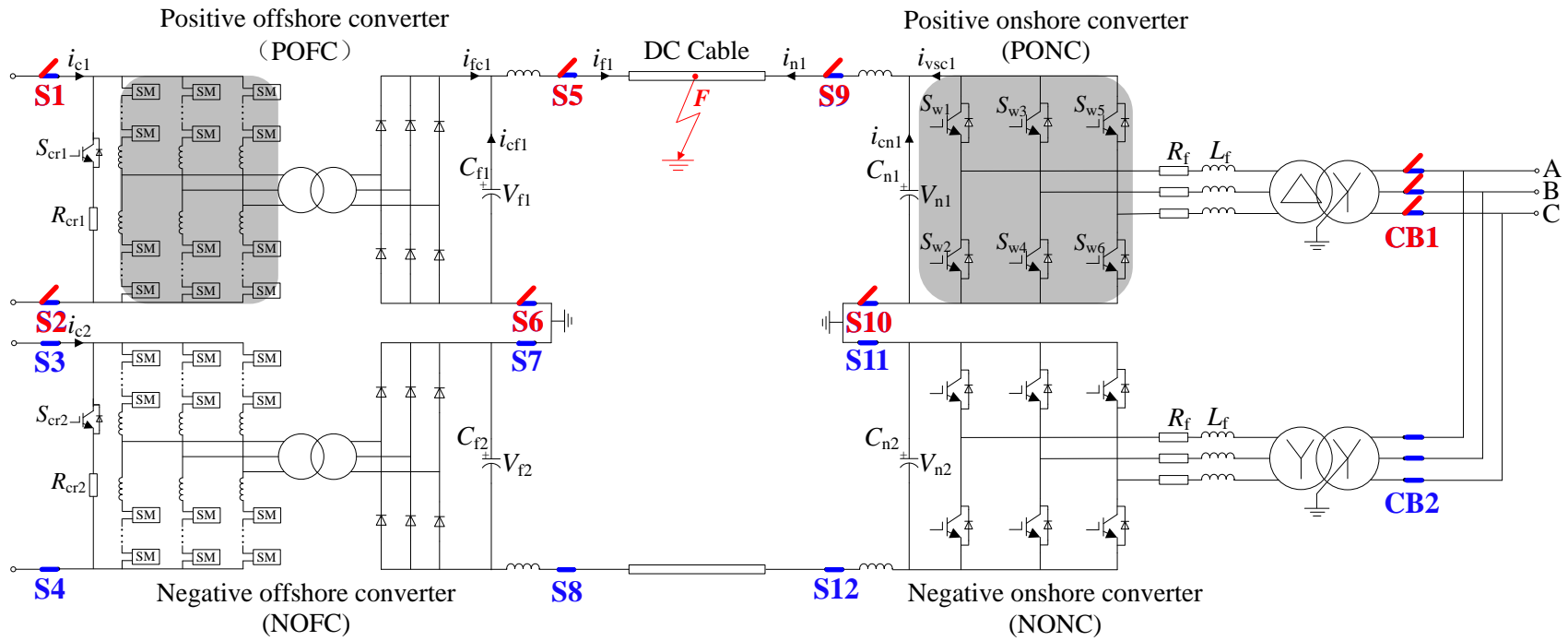- (1) Redundancy for onshore converter
- (2) Redundancy for offshore converter




# DC Grid Control under Faults


## ■ DC grid control under faults

- (1) HVDC system control
- (2) Wind farm control


### Wind turbine (WT) control

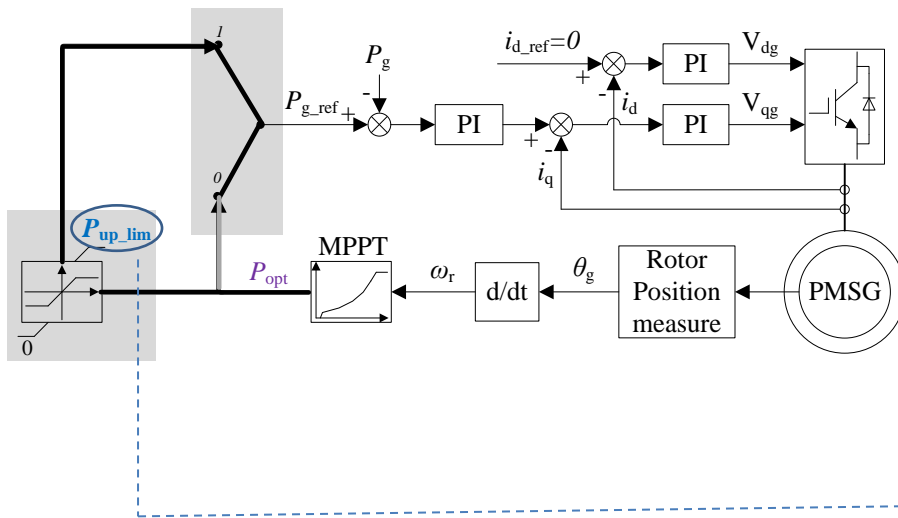

### Chopper resistor control

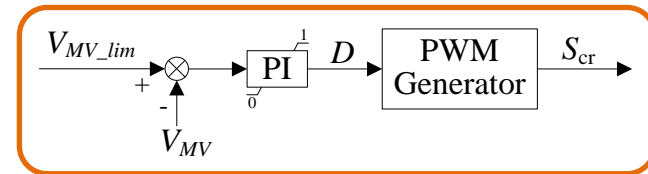

### DC grid control

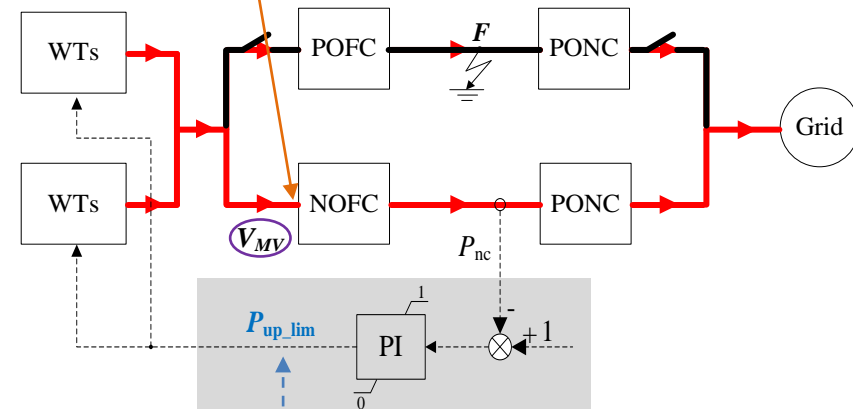



**Thanks!**