

Offshore Wind Farms

Fujin Deng

School of Electrical Engineering

Southeast University

fdeng@seu.edu.cn



Outline

- I. Introduction of Offshore Wind Farms**
- II. Conventional Offshore Wind Farms**
- III. DC grid for offshore wind farms**

1.1 Introduction

Why offshore wind power?

- Better wind source
- High wind speed
- Constant wind speed
- More electricity



**AC Wind
Farm**

**DC Wind
Farm**




1.2 Conventional Offshore Wind Farm

Offshore wind farms

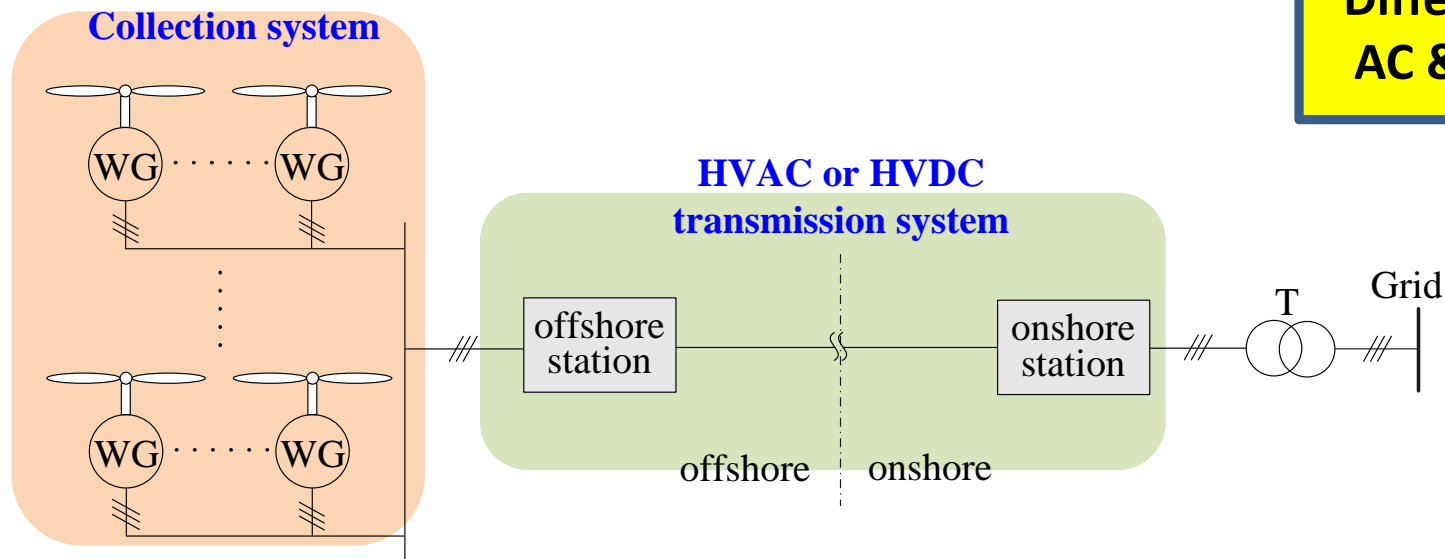- (1) Collection system
- (2) Power transmission system

DC technology advantages

- Reduce cable costs
- No reactive power
- No frequency regulation
- Easy control



**Difference
AC & DC?**

1.3 Wind Farm Configuration


Mature AC Technology

- 33 kV collection AC voltage
- 50 Hz transformer at offshore station

50 Hz or
others?


Variable-frequency control

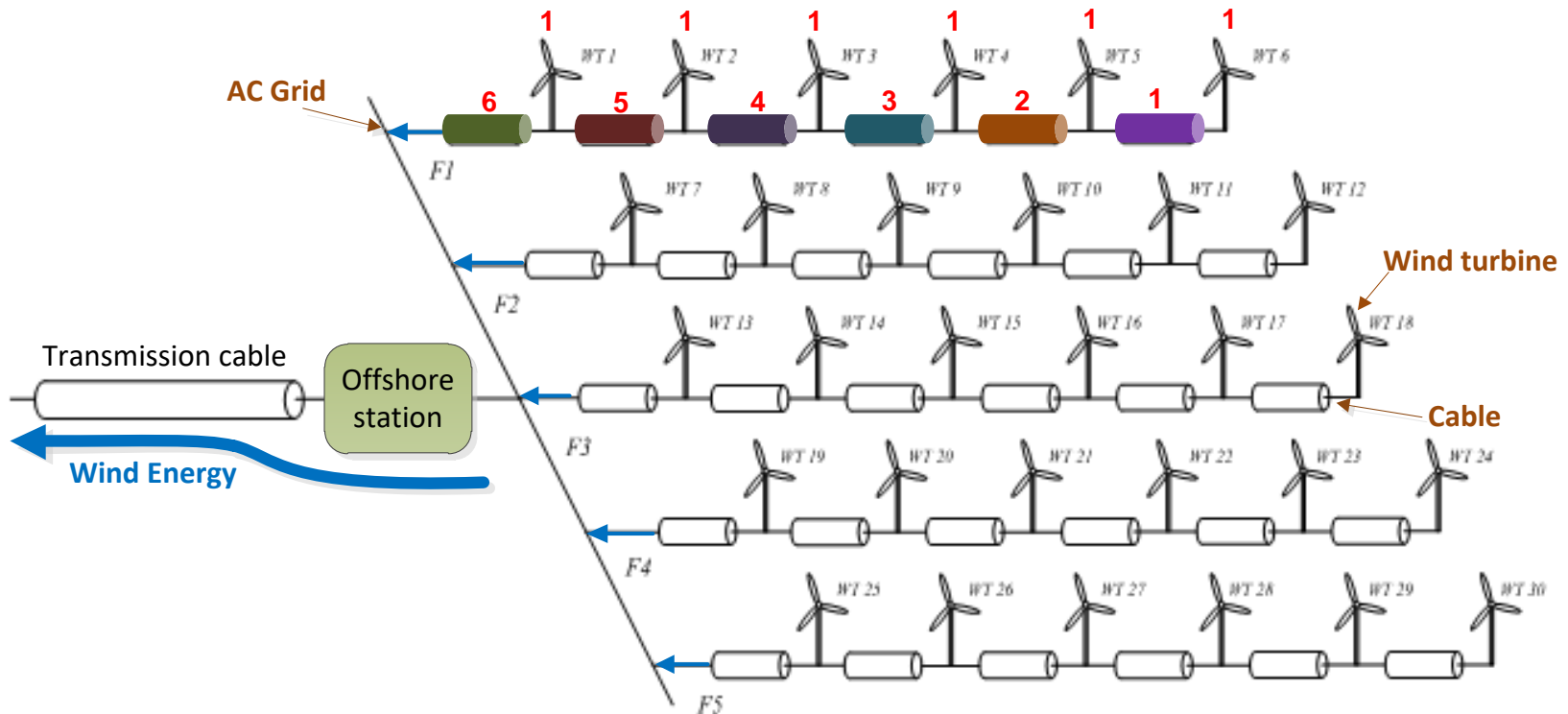- Reduce reactive power loss
- Long distance transmission
- Communications



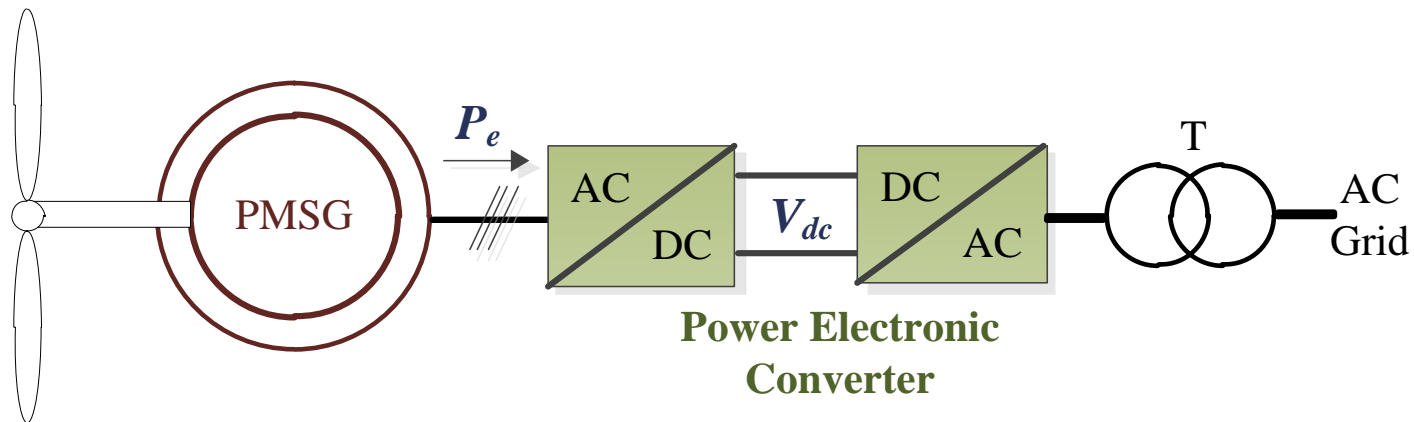2.1 Conventional Wind Turbine in AC Grid

❖ Typical configuration: PMSG-based Wind Turbine with BTB power converter




Advantage

- Robust to grid
- **Suitable for offshore wind power generation**


Disadvantage

- Full rated power
- High cost

2.1 Conventional Wind Turbine in AC Grid

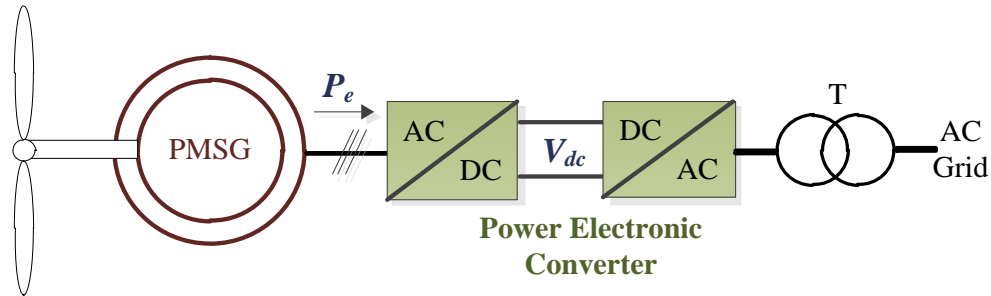


□ 2-Level

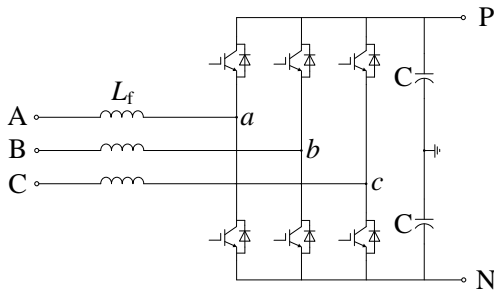


- Low voltage (e.g. 380V, 690V)
- High harmonics

□ 3-Level

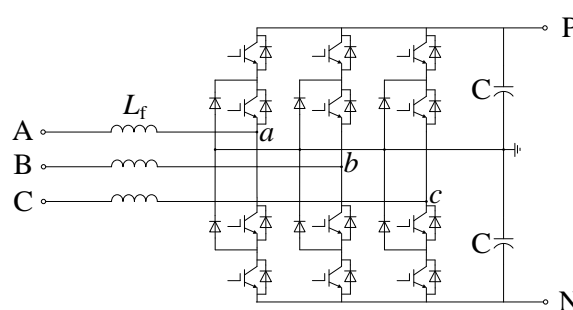

- Medium voltage (e.g. 3 kV)
- Low harmonics
- Capacitor voltage balancing issue
- Power device loss


□ Multi-Level

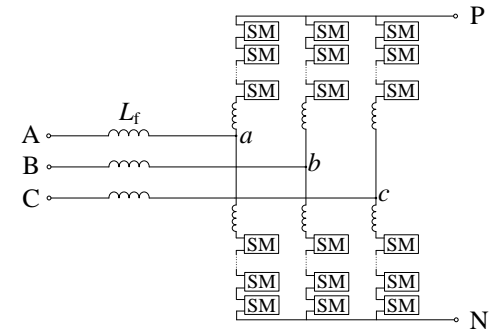

- High voltage (e.g. >3 kV)
- Low harmonics
- Capacitor voltage ripple issue
- Size issue

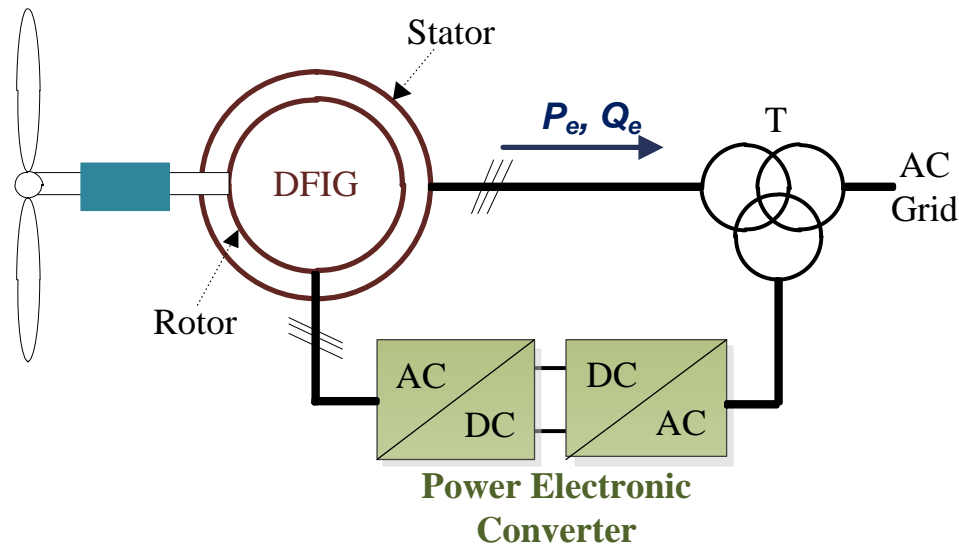2.1 Conventional Wind Turbine in AC Grid

❖ Typical configuration: DFIG-based Wind Turbine with BTB power converter



Advantage


- Small rated power
- Low cost

Disadvantage


- Easily affected by grid (because the stator is directly connected to the grid)

2.1 Conventional Wind Turbine in AC Grid


❖ Solutions for Grid Disturbance Issue:

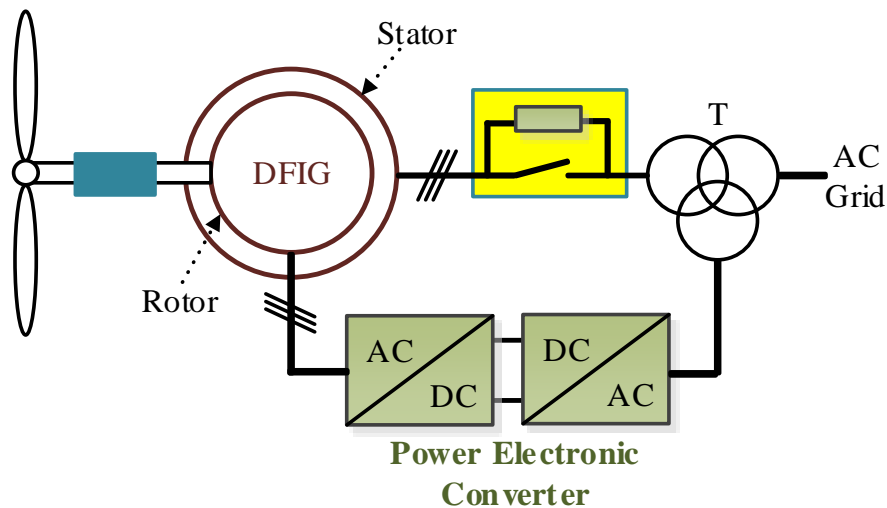


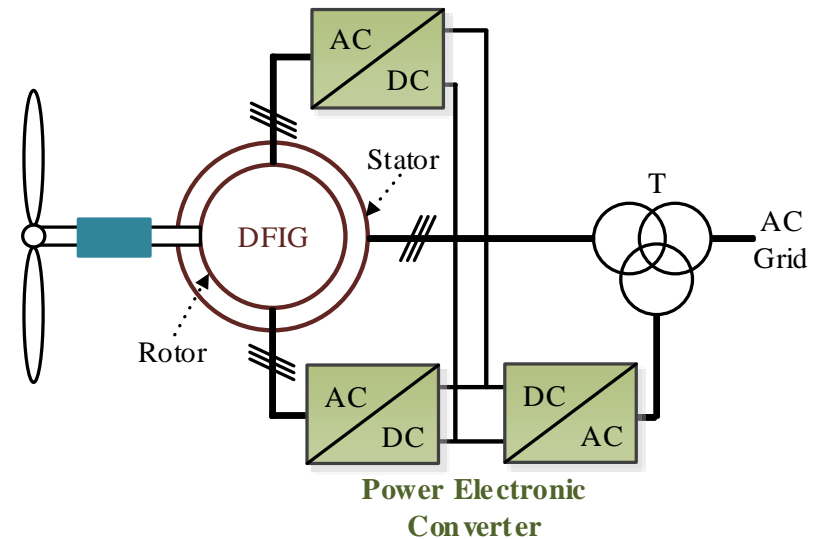- Normal operation:
Resistor is bypassed
- Grid disturbance situation:
Resistor is inserted into the grid between the stator and grid




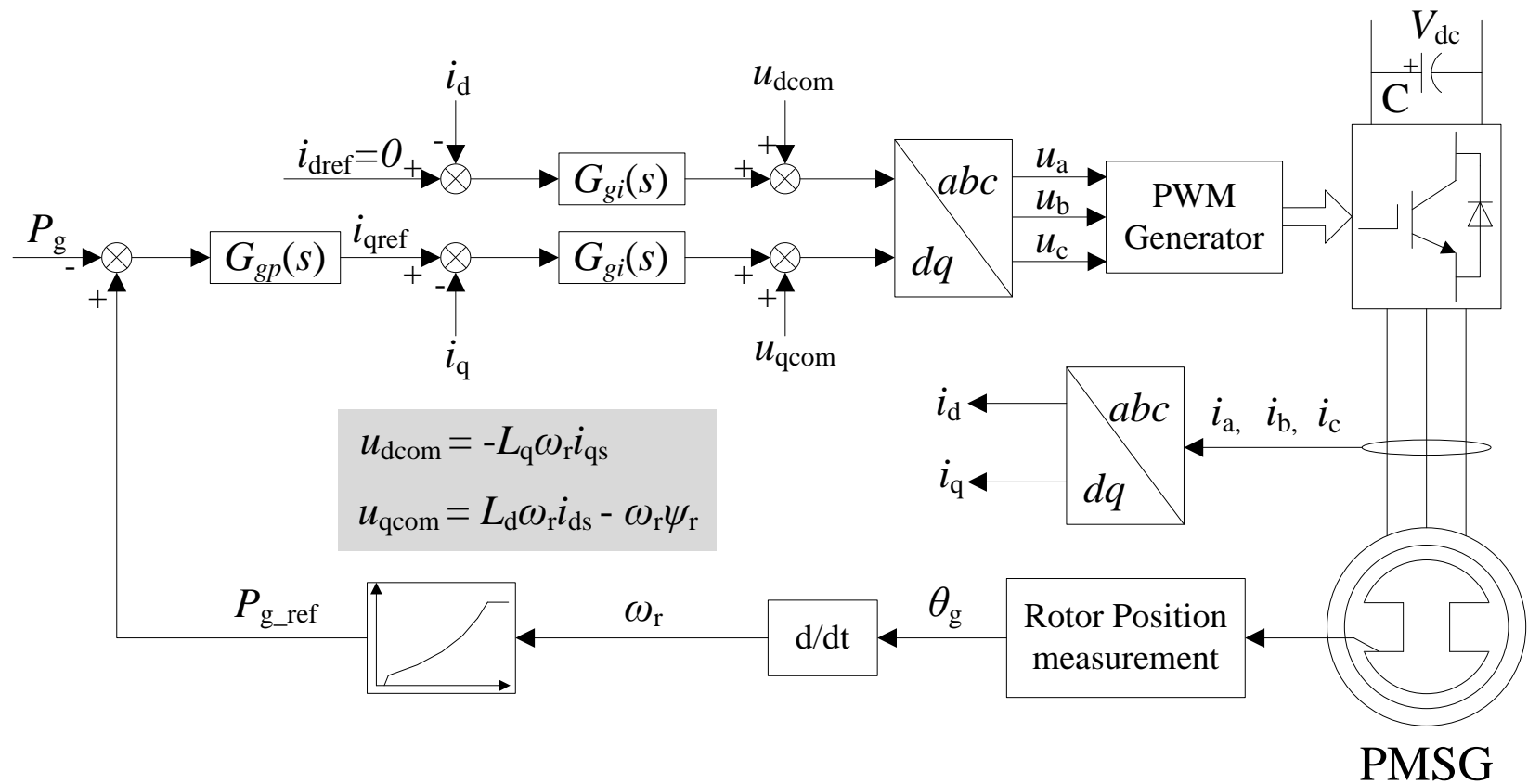- Normal operation:
AC/DC connected to rotor to produce the flux
- Grid disturbance situation:
AC/DC connected to rotor to regulate the flux



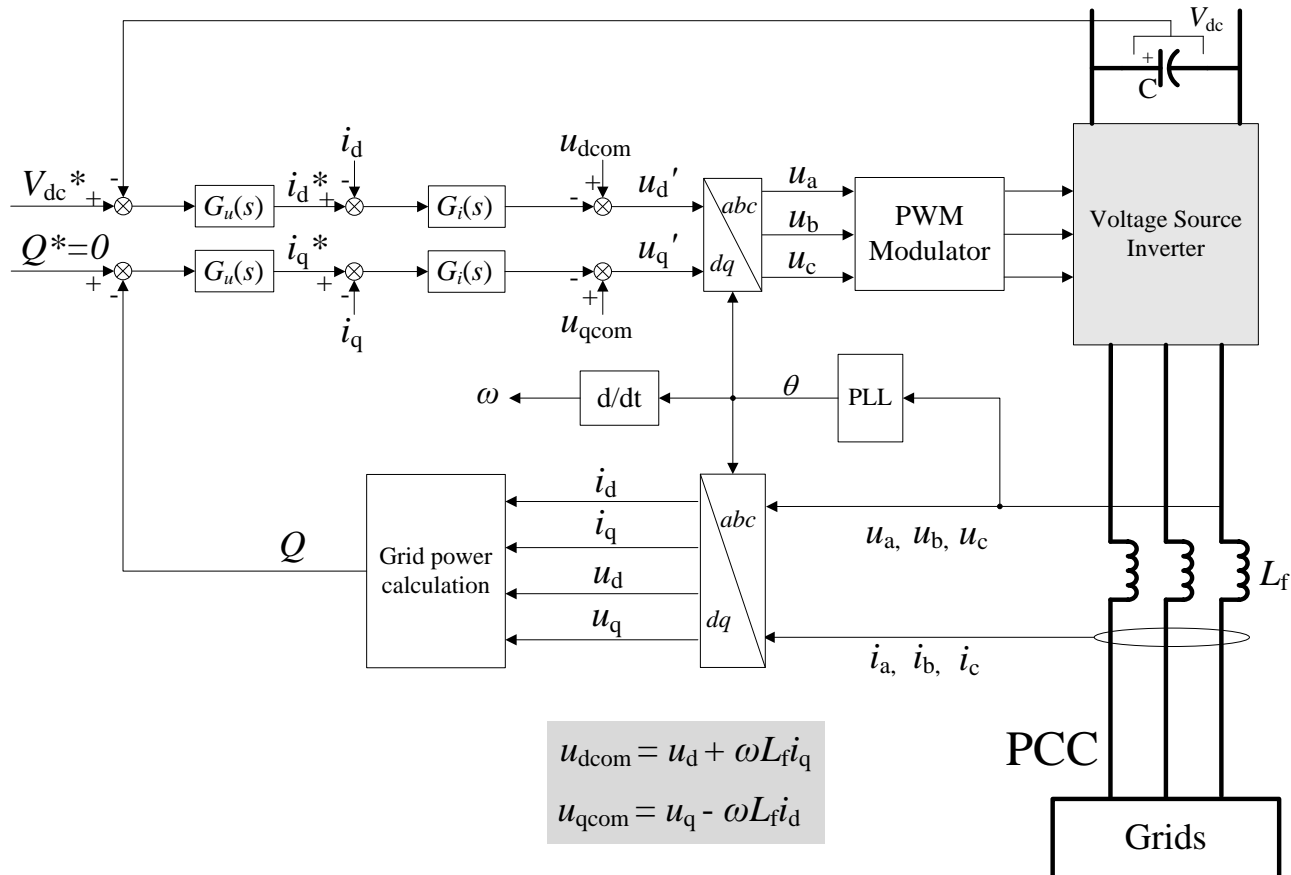


2.2 Other Wind Turbines - 1

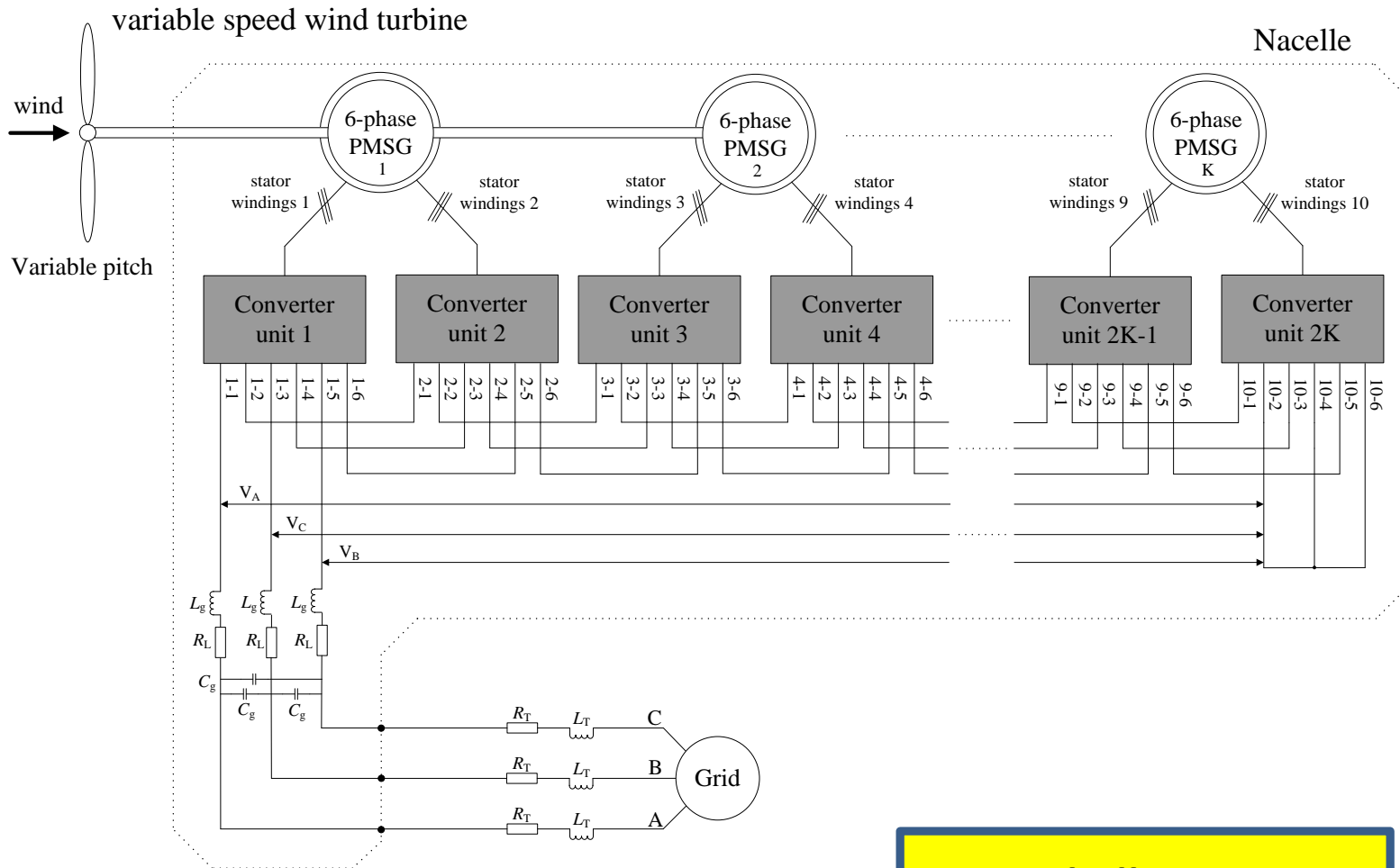

Challenge:
High grid voltage?


2.2 Other Wind Turbines - 1

Converter unit topology:

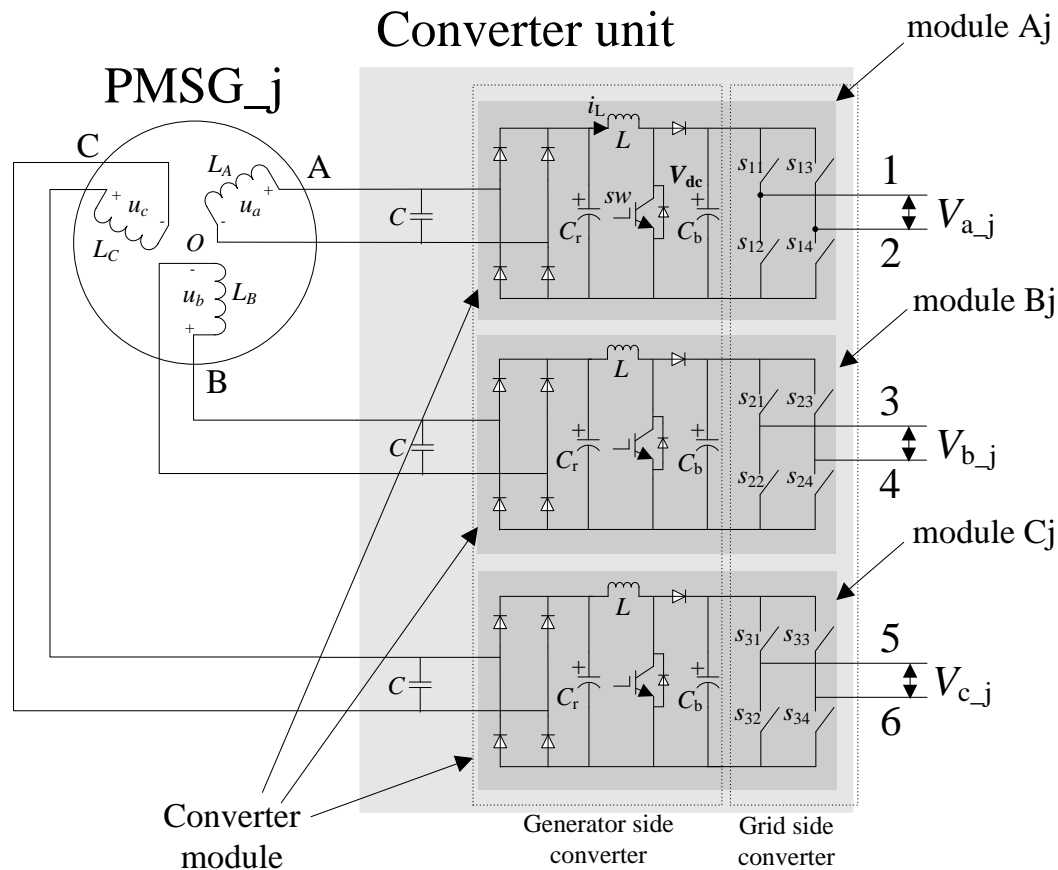

2.2 Other Wind Turbines - 1

Cascaded multilevel converter

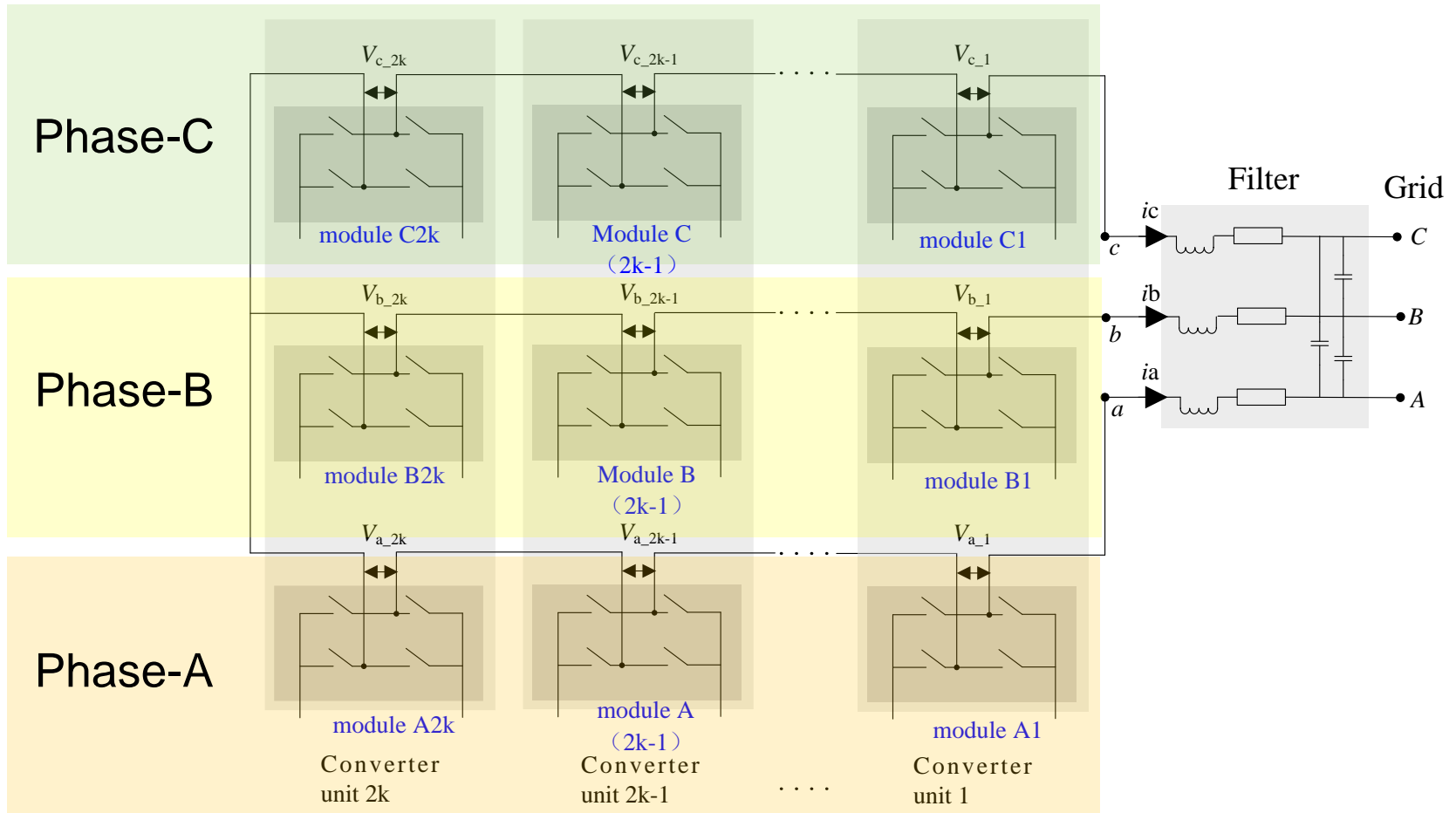


Control strategy



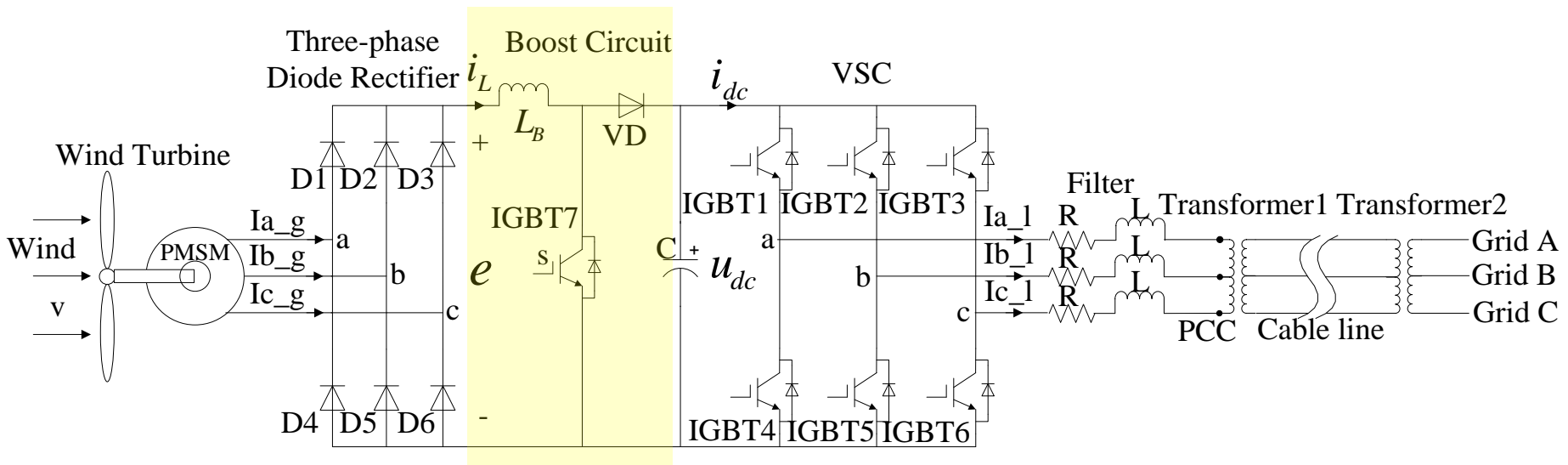
2.3 Other Wind Turbines - 2

- Permanent Magnet Synchronous Generator (PMSG)
- Three-phase Diode Rectifier
- Boost Converter
- Voltage Source Converter (VSC)




Conventional Control


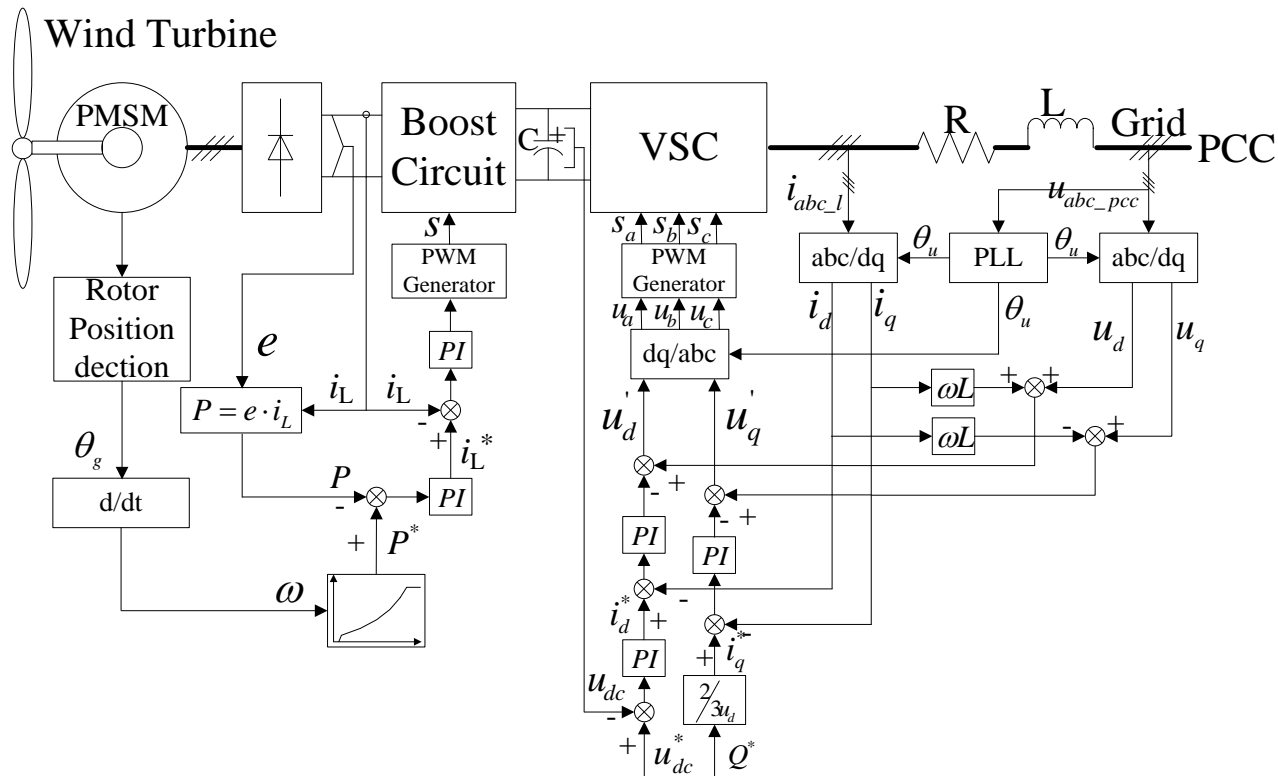
- Boost DC/DC Converter → P
- Voltage Source Converter → Udc & Q



Grid Code (Low Voltage)

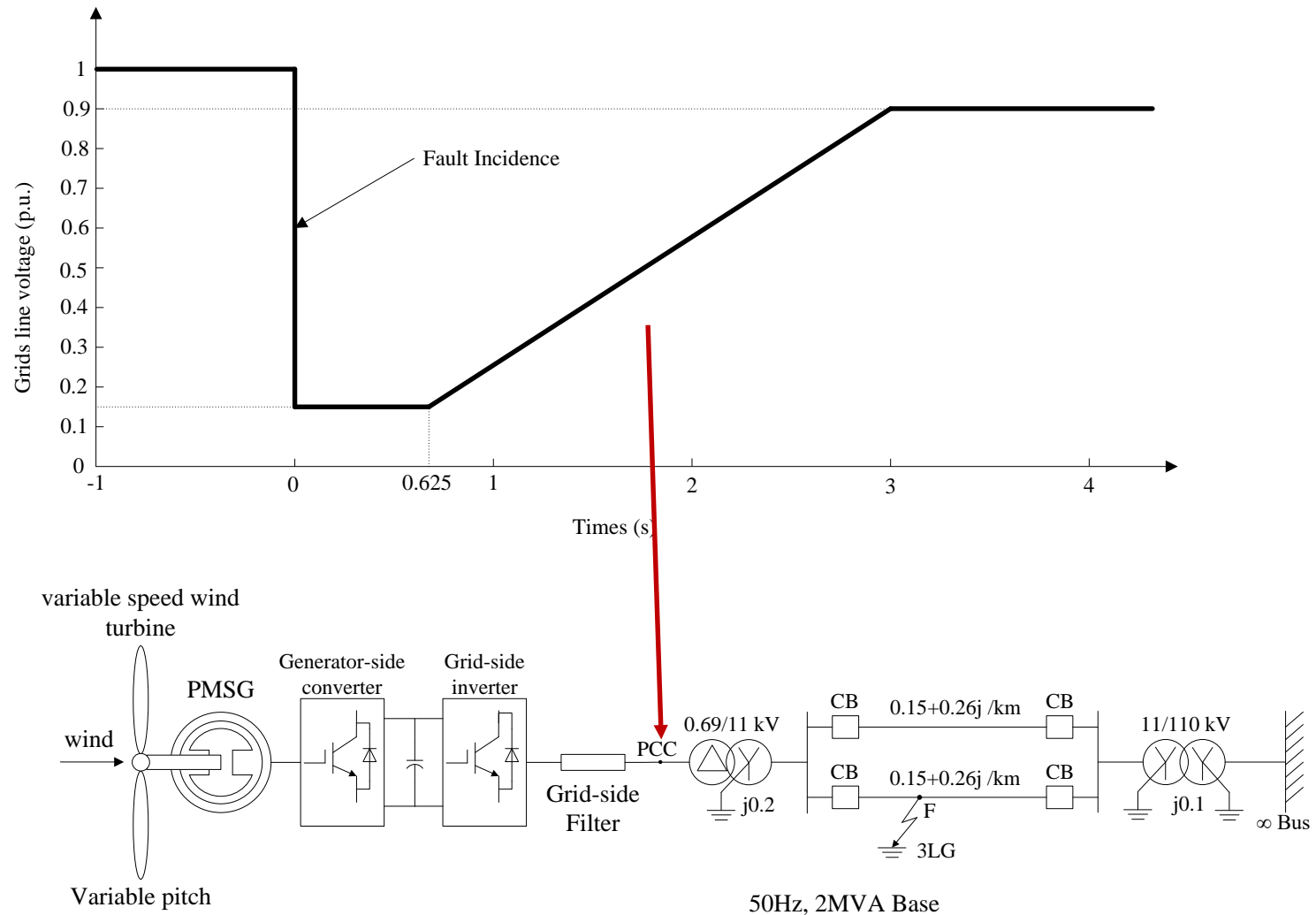


DC-link voltage ripple

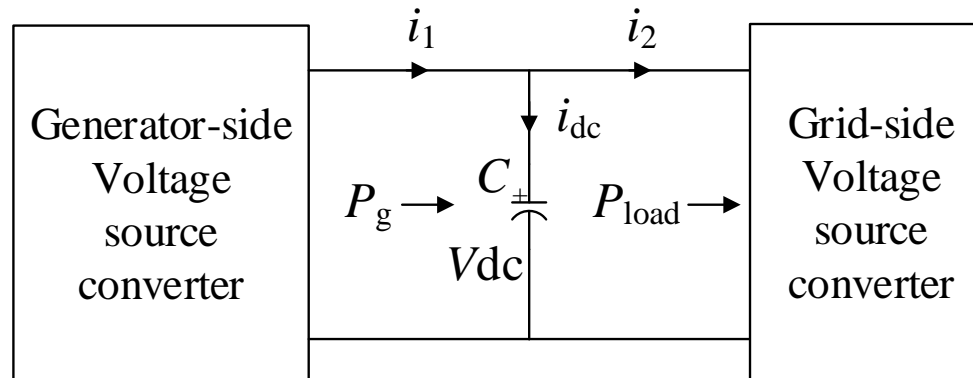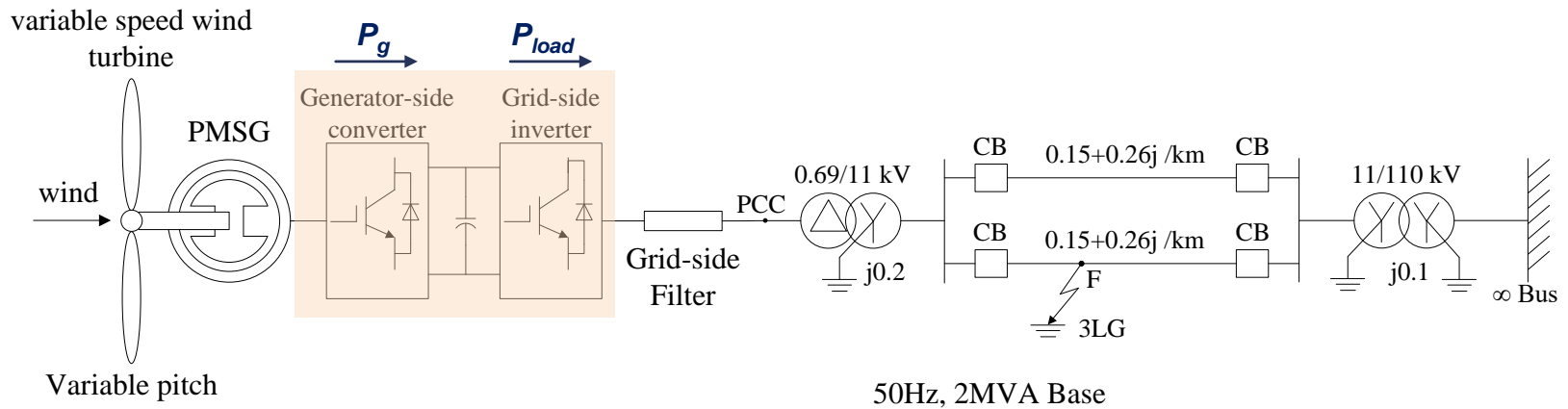

Control for DC-link Ripple Elimination:

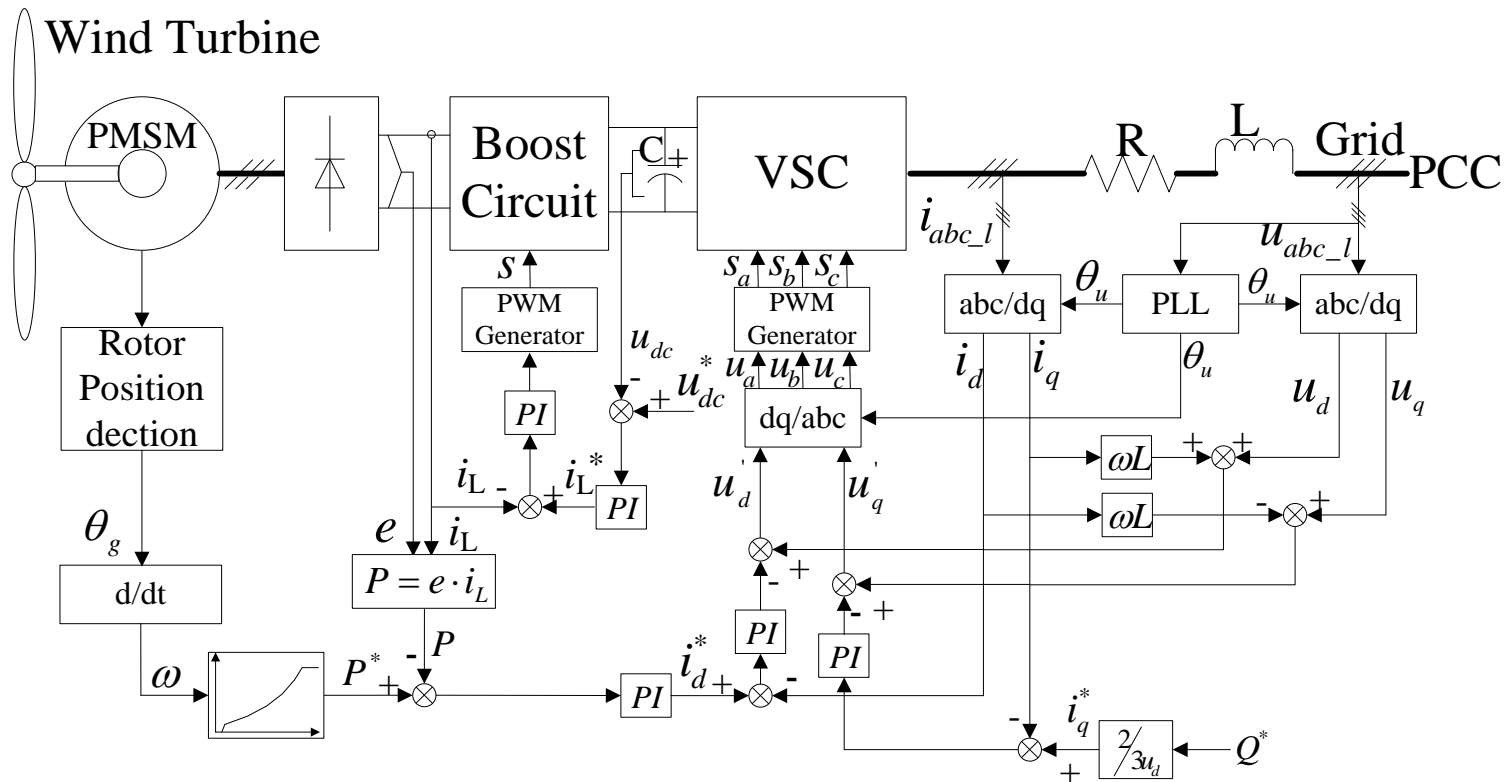
- Boost DC/DC Converter → U_{dc}
- Voltage Source Converter → P & Q




Simulation


Condition:

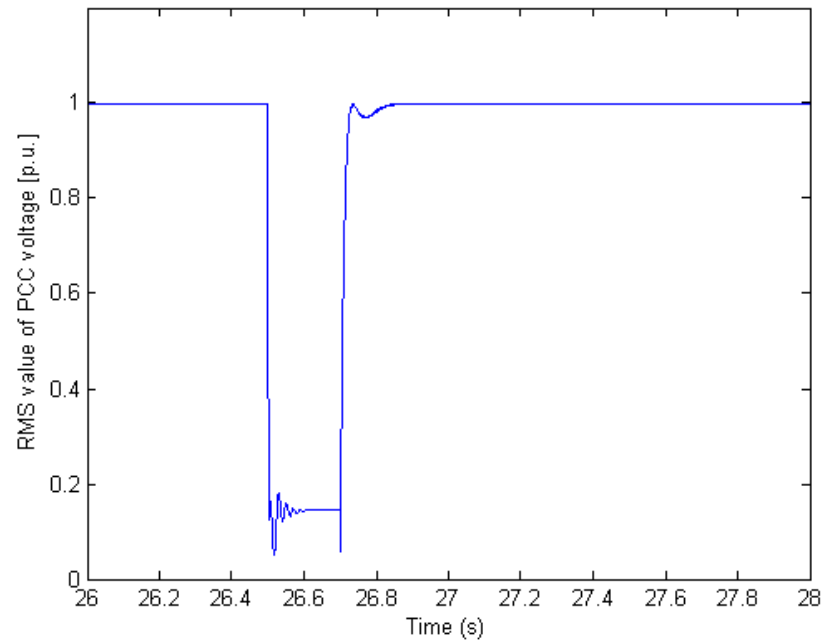- Wind speed is constant as 11m/s
- PCC voltage dips to 15% of rated value




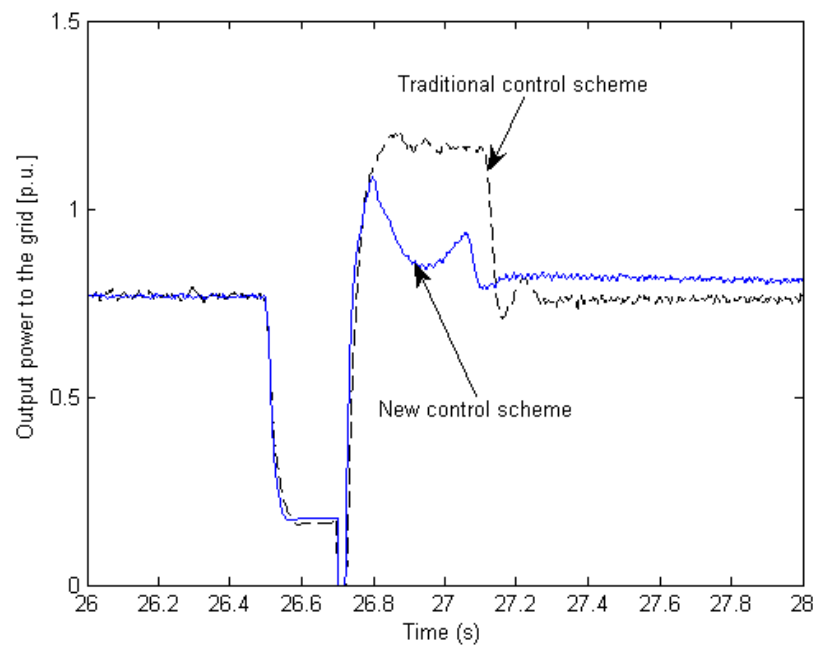


Output power to the grid

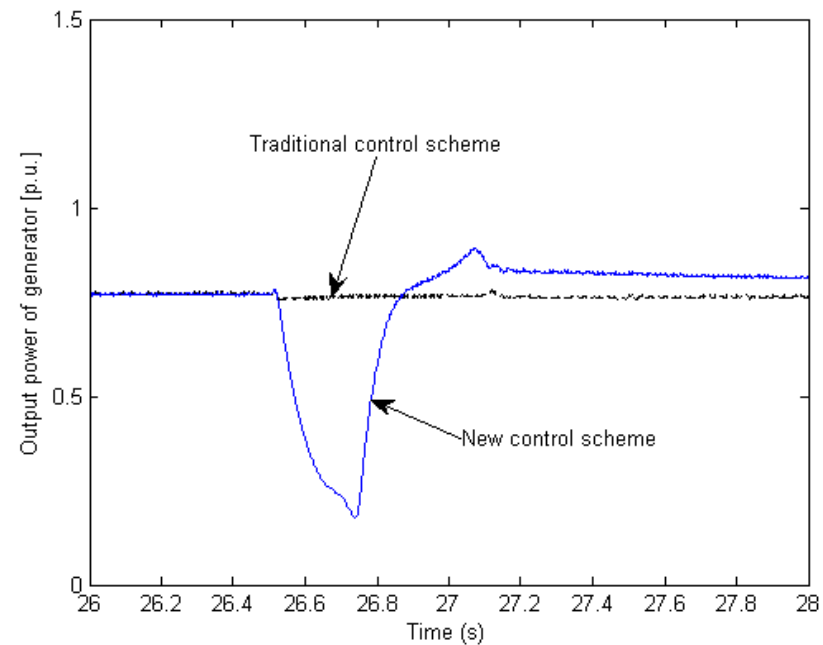


Generator output power

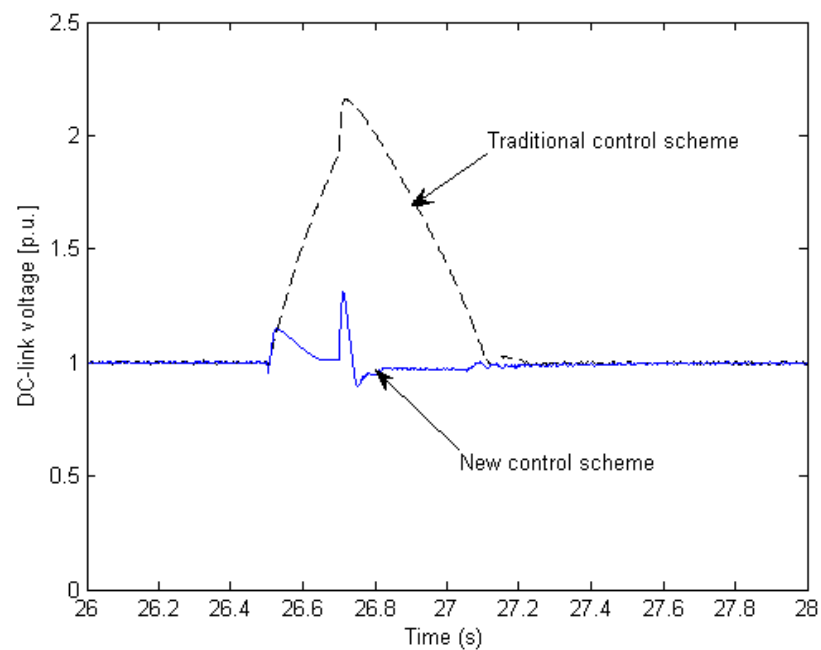


DC-link voltage

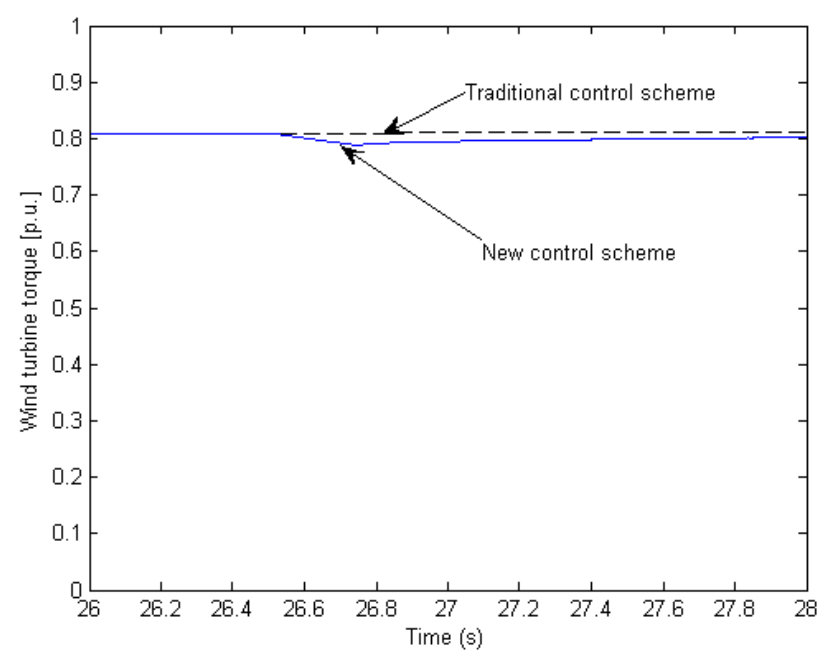


Wind turbine torque

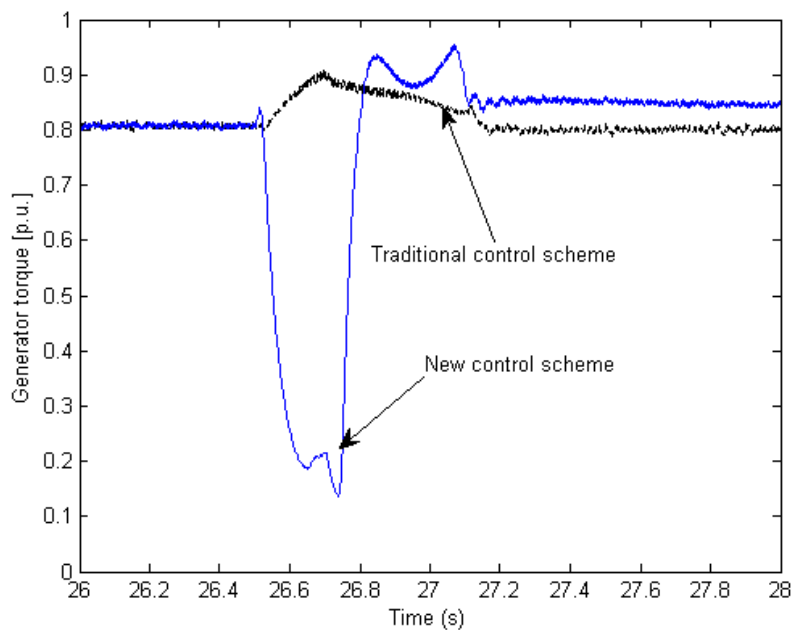

Generator electromagnetic torque

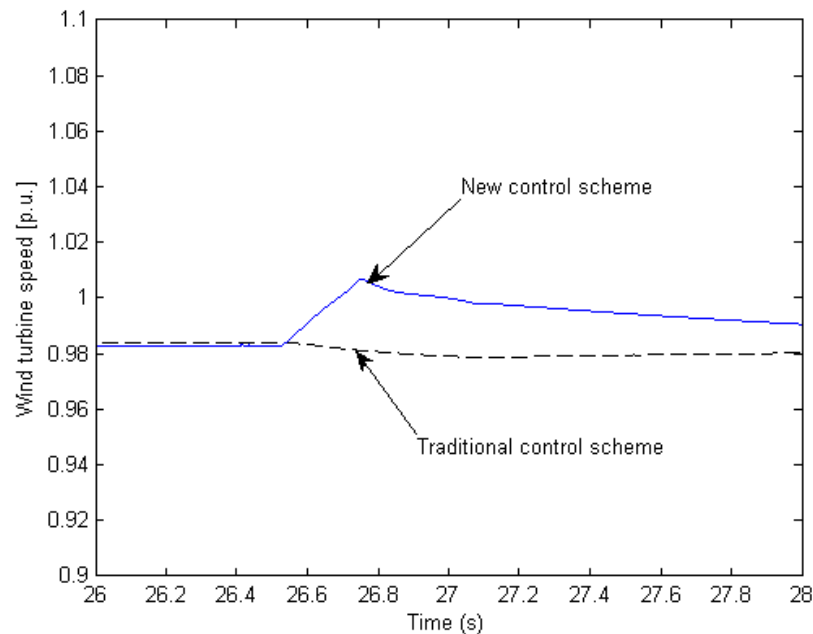


Wind turbine speed

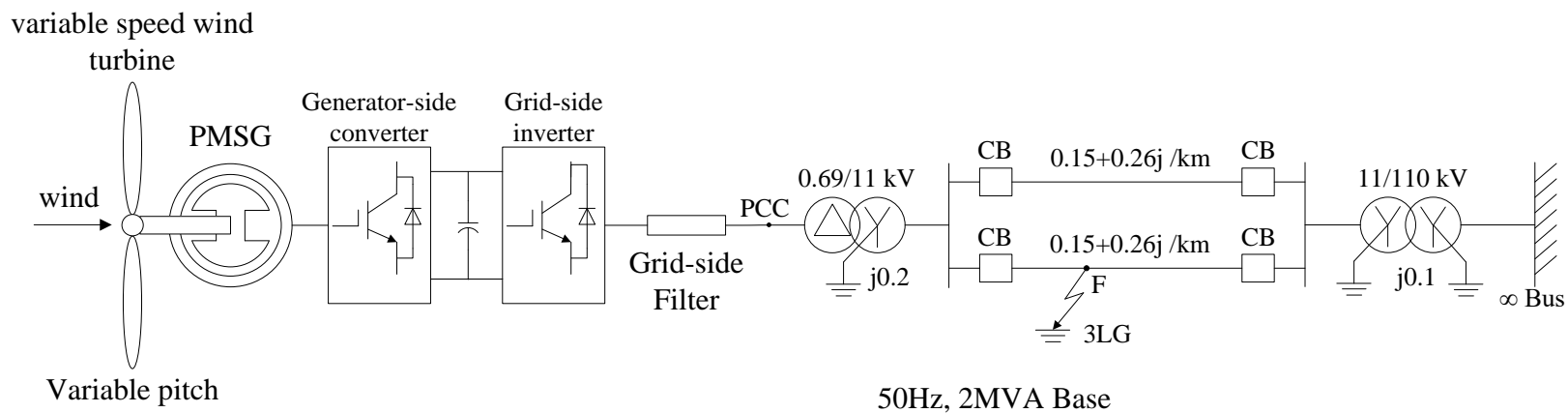


2.4 Other Wind Turbines - 2

■ Wind Turbine in Stand-Along System

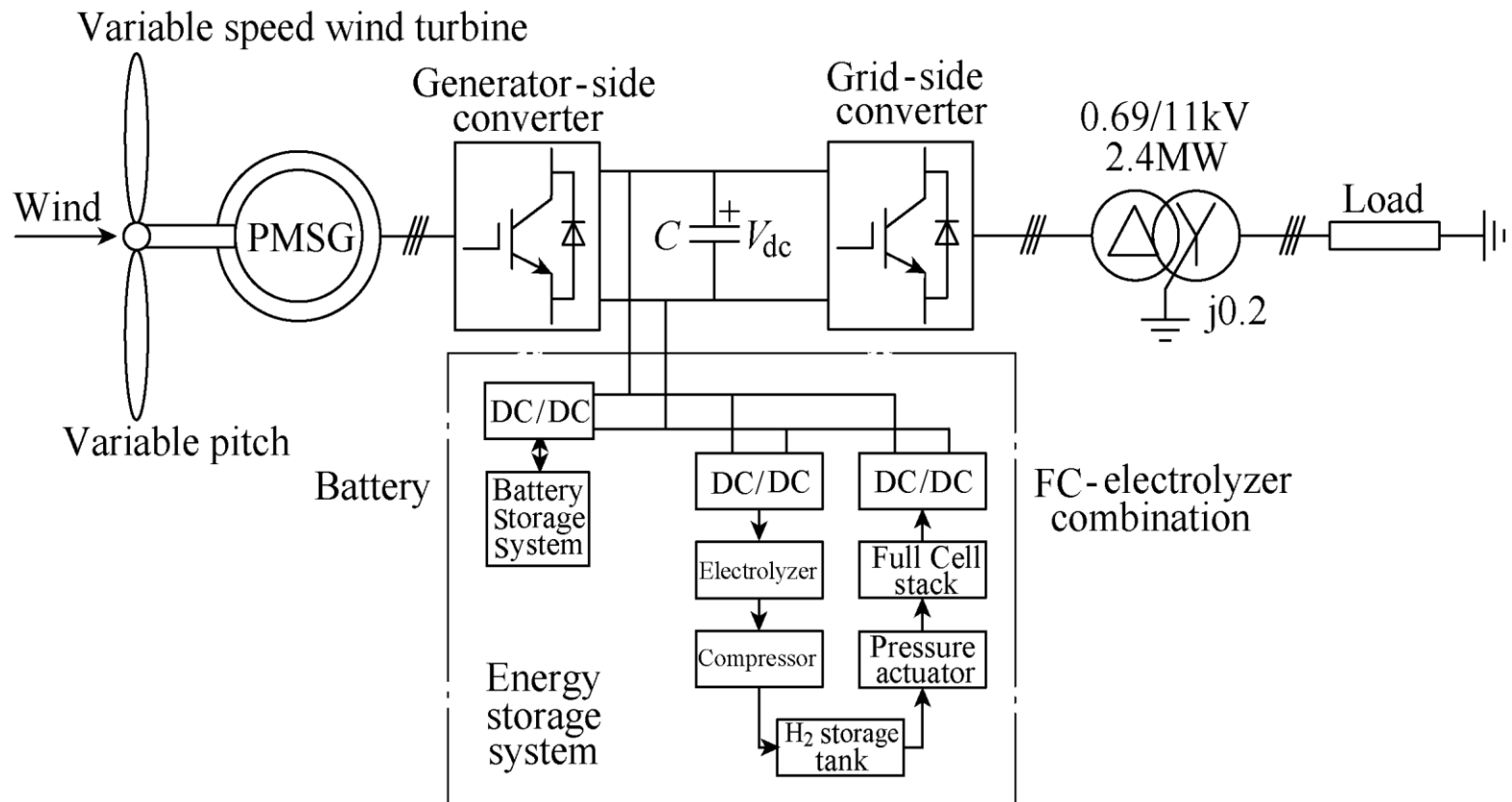


■ Selection of Wind Turbine


● House power consumption in 2019

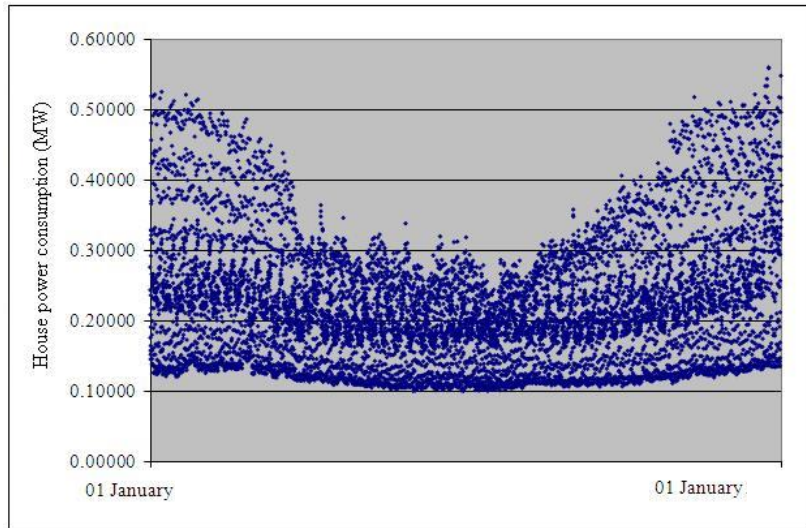

● Wind power production in 2019

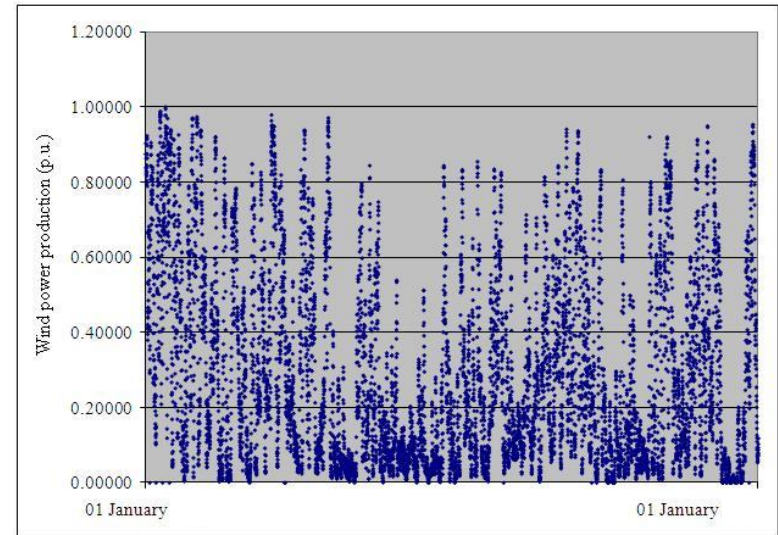

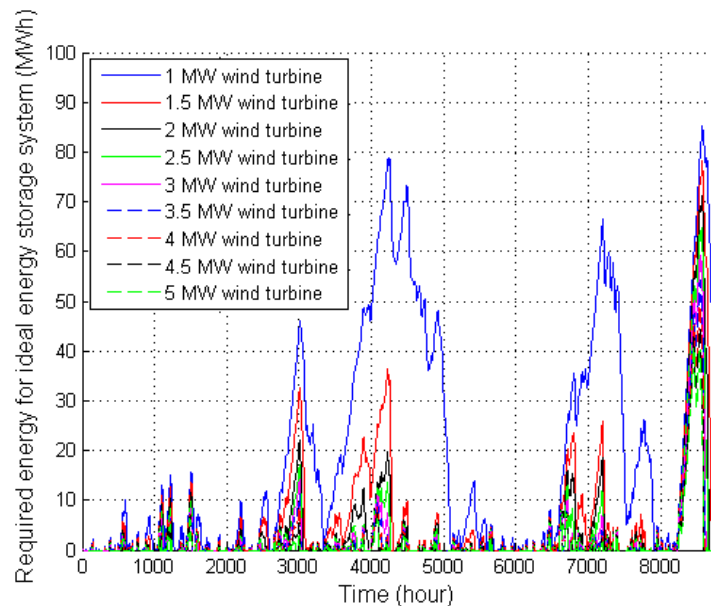● Energy required for ideal energy storage system




Selecting wind turbine size based on


- ✓ Size of energy storage system
- ✓ Cost of WT
- ✓ Cost of ESS

■ Battery Energy Storage System

● DC/DC Buck/Boost Converter

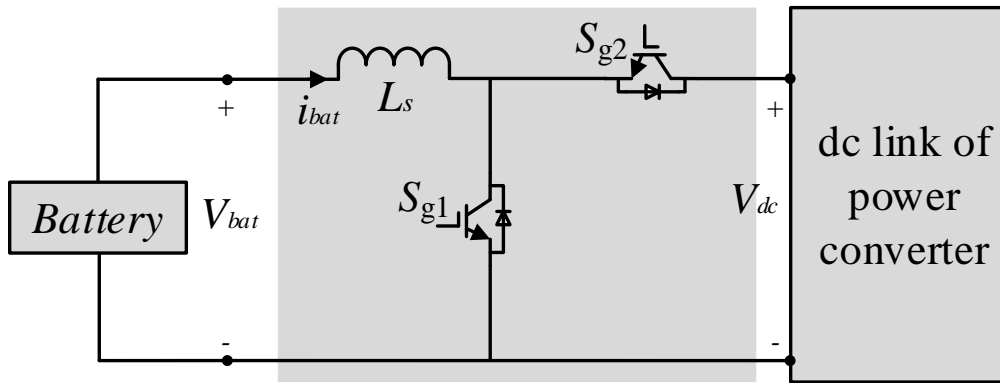

● Third-order battery model


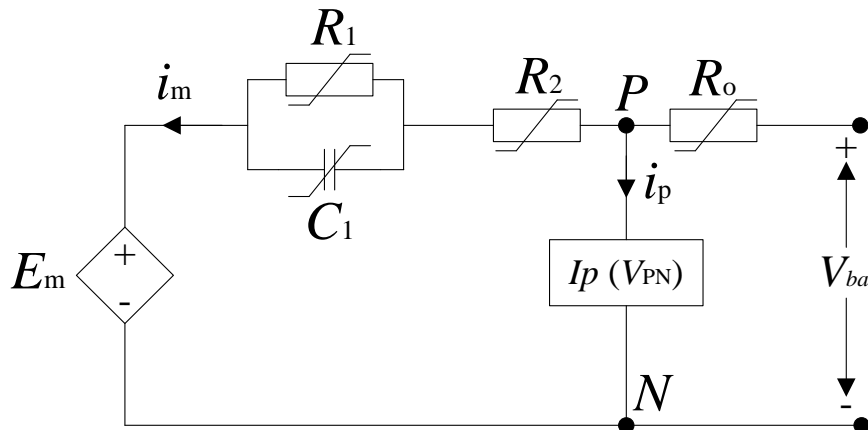


Researches



- DC/DC converter
- Control of DC/DC converter
- Cooperation control of Generator-side converter, DC/DC converter, grid-side converter
- Lifetime analysis of battery
- Control optimization for battery lifetime

2.5 Other Wind Turbines - 3

❖ WT configuration 1 (Multiple-windings)

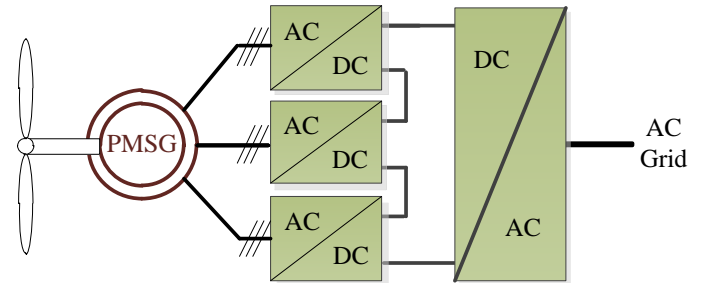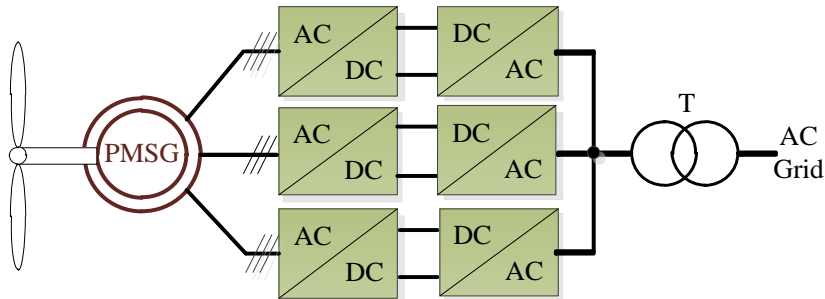


❖ WT configuration 2 (Multiple-windings)

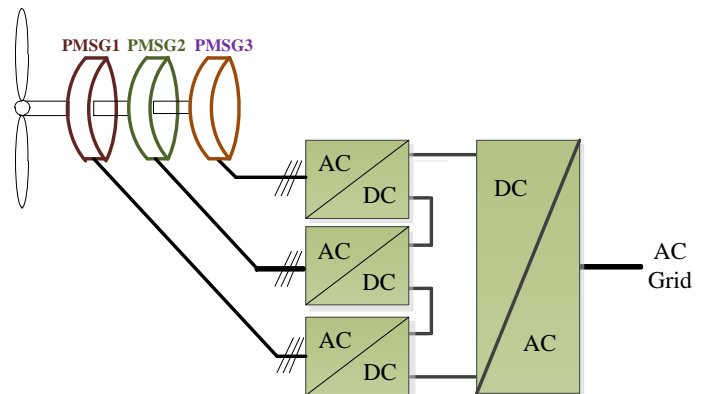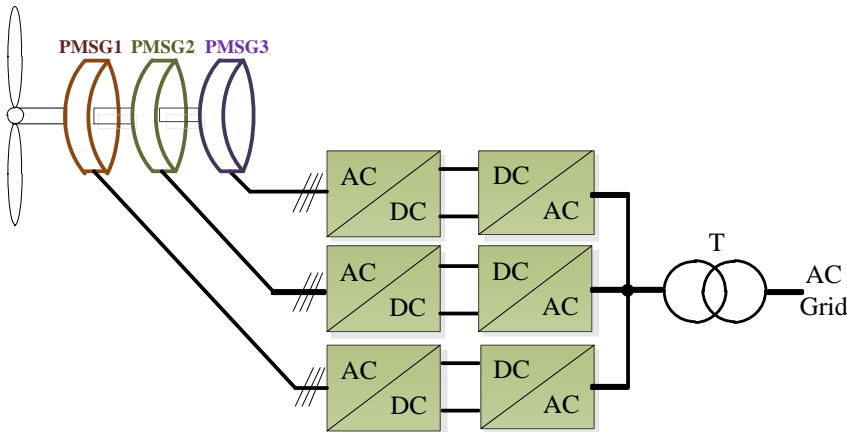

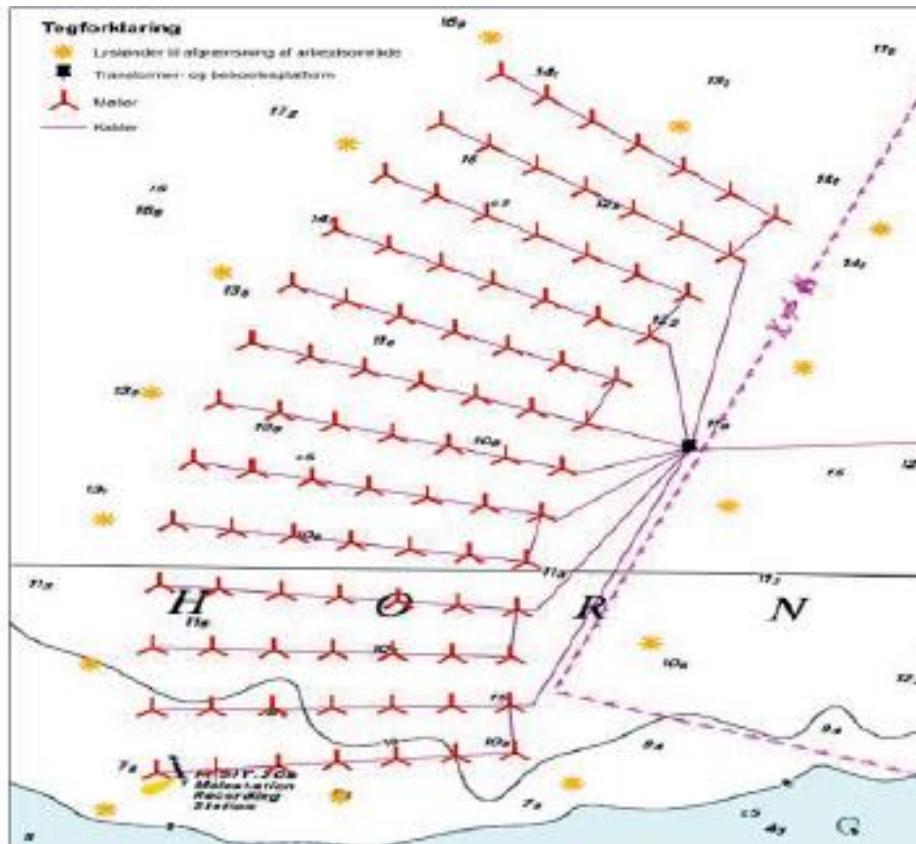2.6 Wind Farm Configuration

Researches point

- Topologies of wind farms → Optimization
 - Control of wind turbines → Optimization
- Optimization



Main effects:


- Topology affects the wind power capture
- Topology affects the size of cables and power losses in collection system
- Control of wind farm affect the optimal wind power capture
- Control of wind farm affect the power loss

3.1 DC Grid for Offshore Wind Farms

Main researches

- Wind turbine
- HVDC system
- Cable faults


Wind turbine
configuration
and control

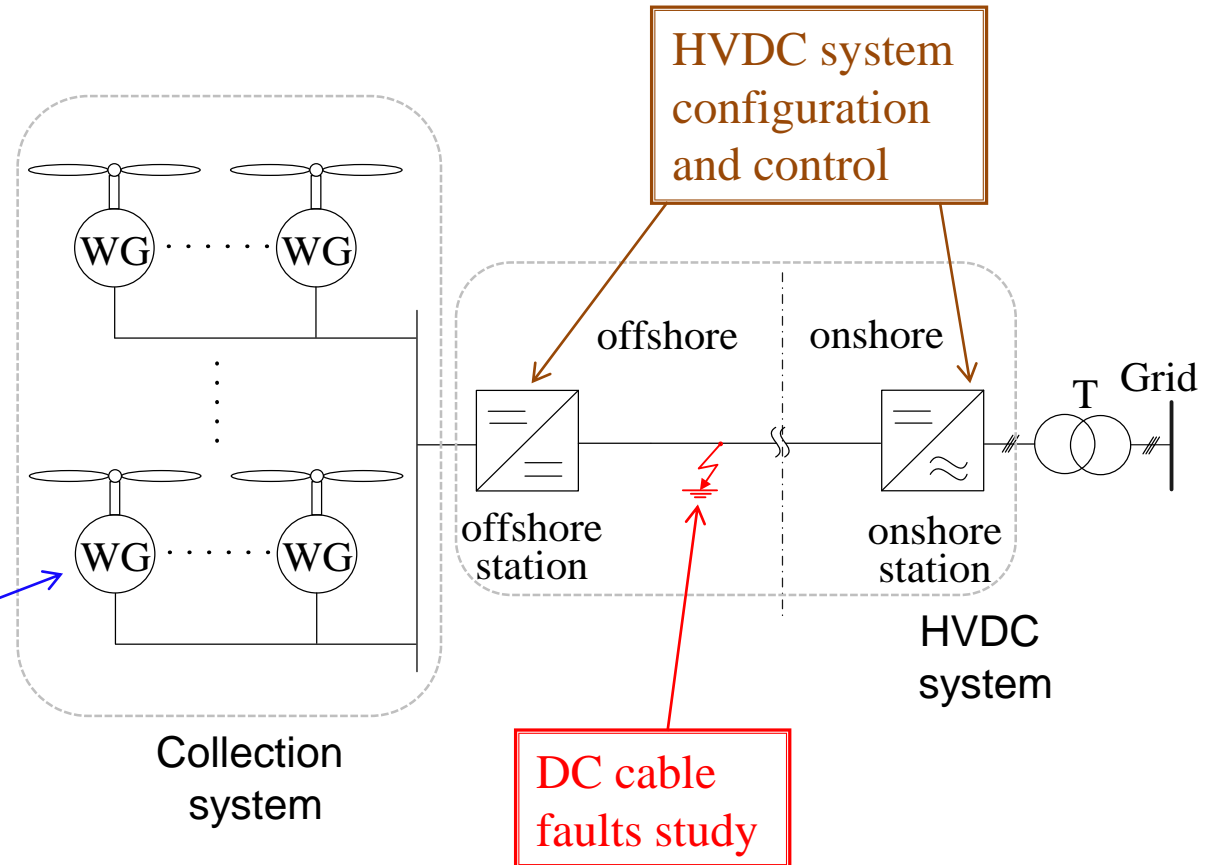

3.2 Wind Turbine for DC Grid


1. Wind turbine configuration I

3-L NPC converter
+
DC/DC converter

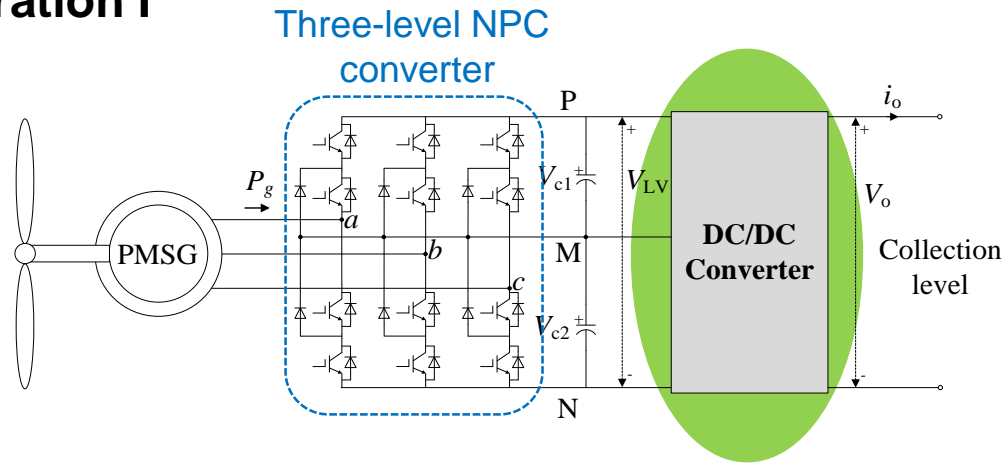

2. Wind turbine configuration II


Diode rectifier
+
DC/DC converter

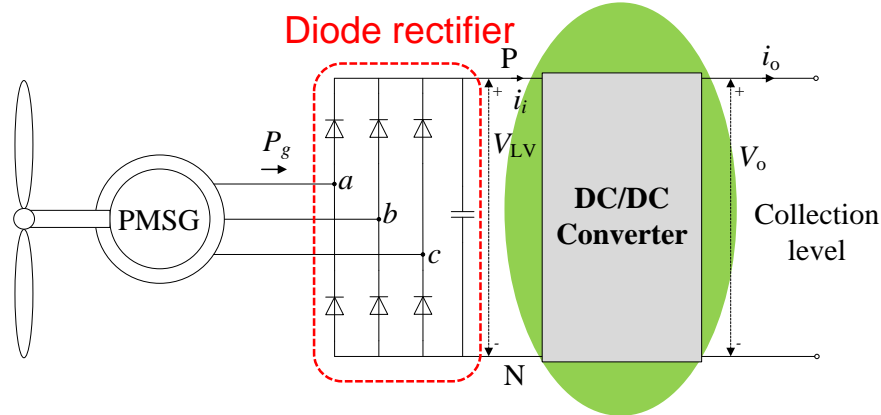

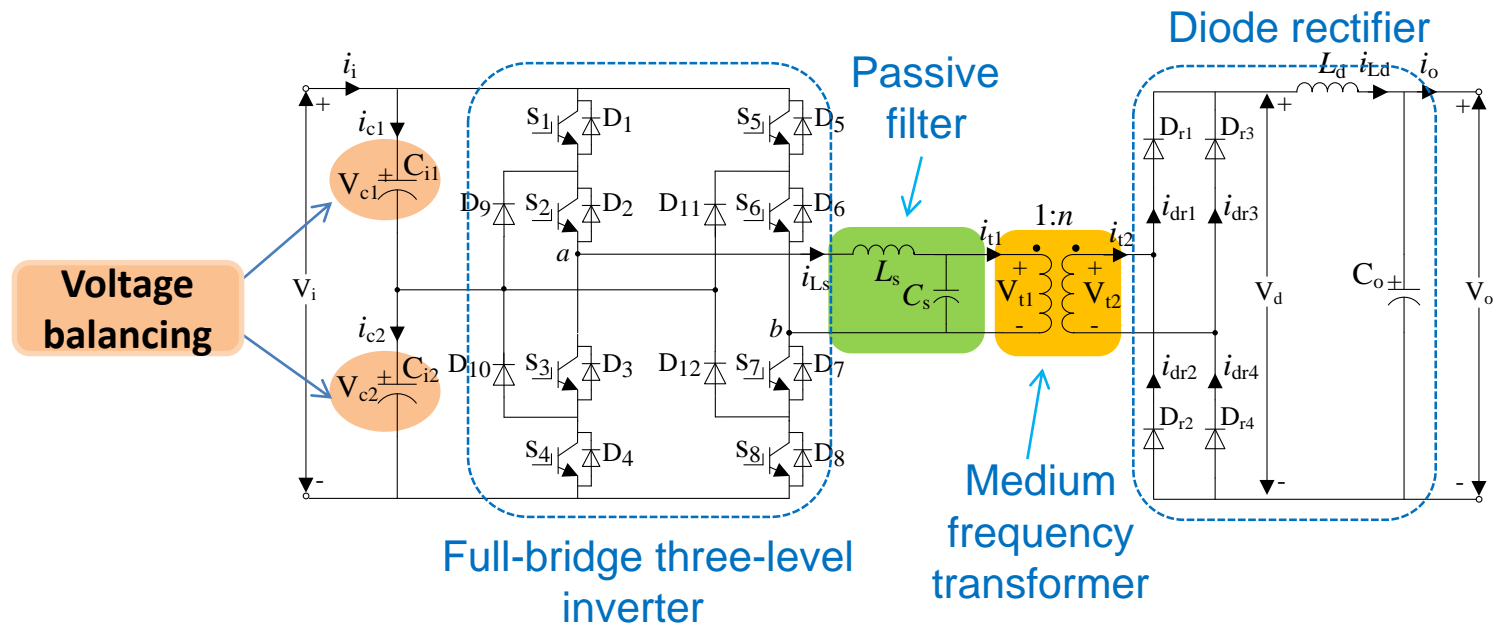3.3 A DC/DC Converter


Isolated full-bridge three-level DC/DC converter

- Isolated DC transformer
- 3-level configuration
- Medium switching frequency




Modulation Strategy


Modulation mode I

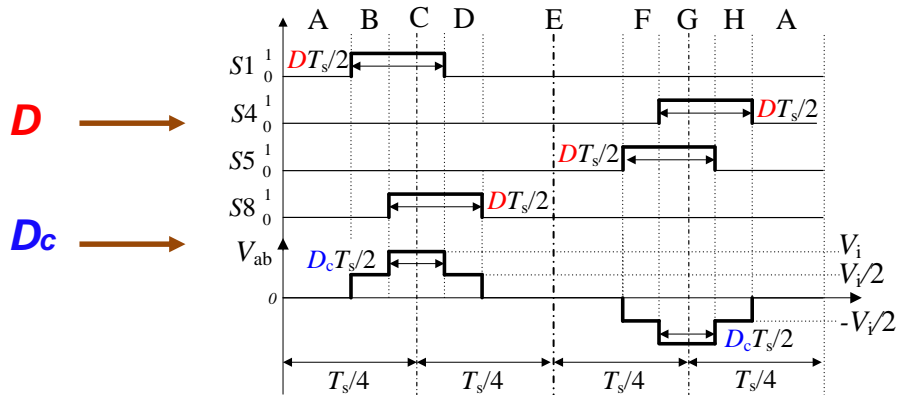

Full-bridge 3-L inverter

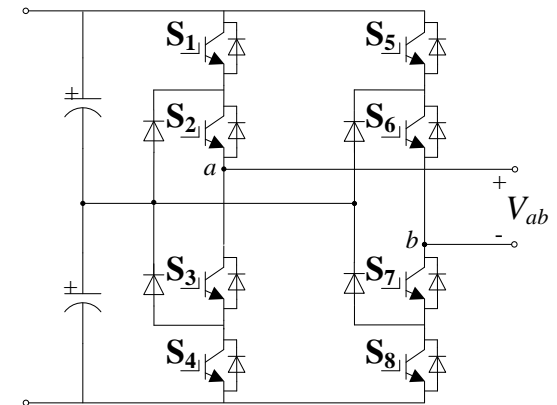

Modulation mode II

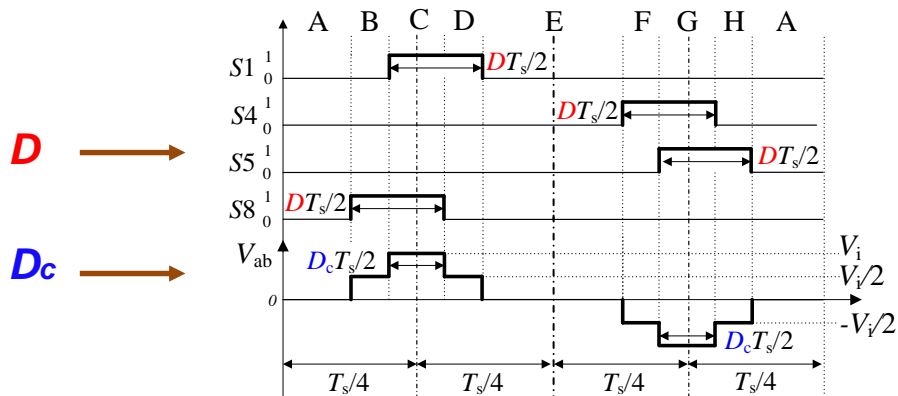


$$S_3 = \overline{S_1} \quad S_6 = \overline{S_8}$$




$$S_2 = \overline{S_4} \quad S_7 = \overline{S_5}$$

DC Capacitor Voltage Balancing Control

Modulation mode I

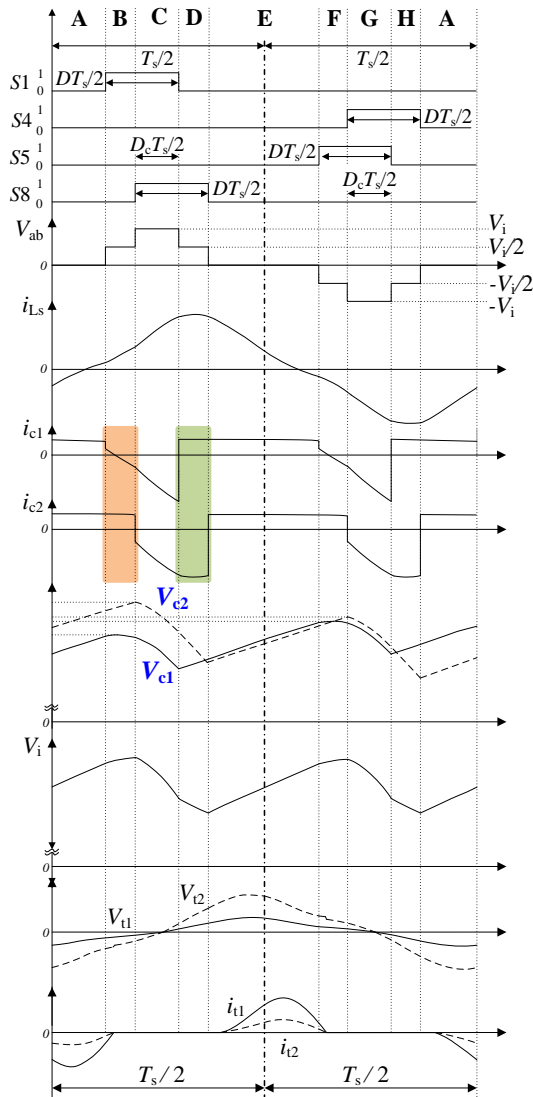

Modulation mode II

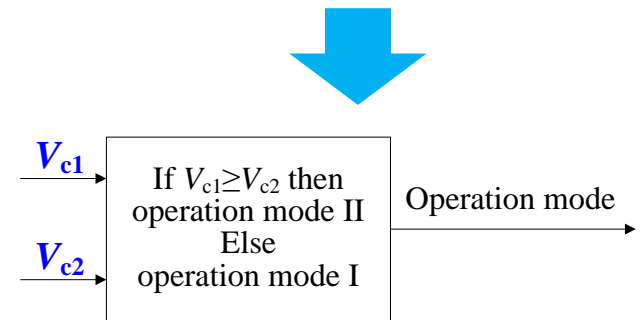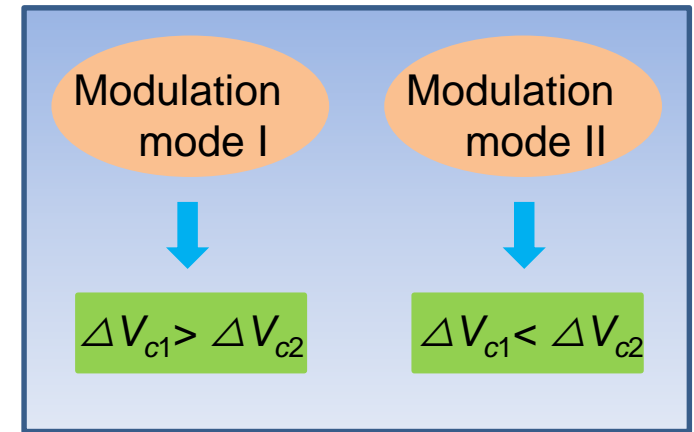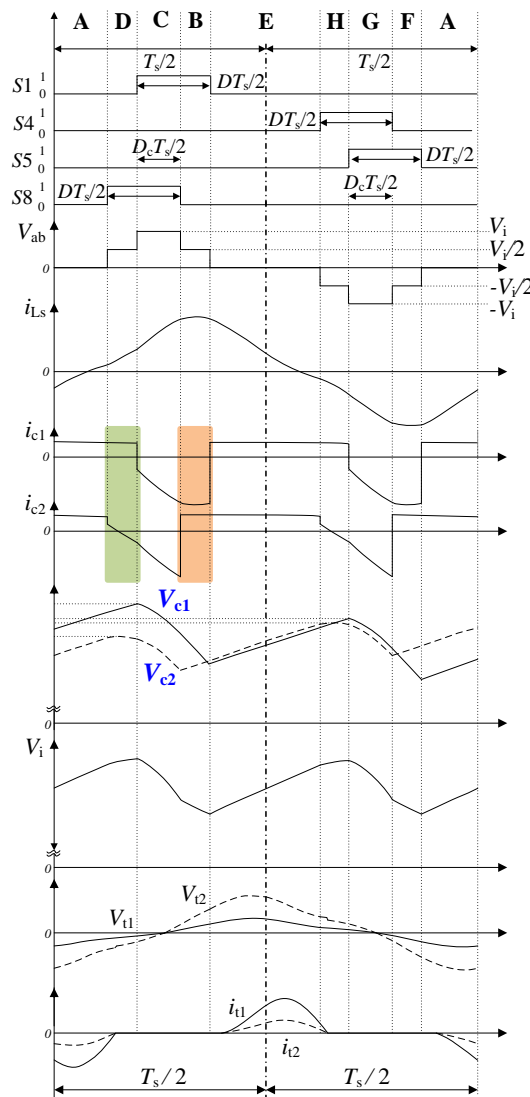

Wind Turbine Control 1


1. Control of wind turbine configuration I

(1) Generator-side converter control

- Optimal power control P_{ref}
- Reactive current control $i_{sd_ref}=0$




(2) Grid-side converter control

- DC-link voltage control V_{dc_ref}



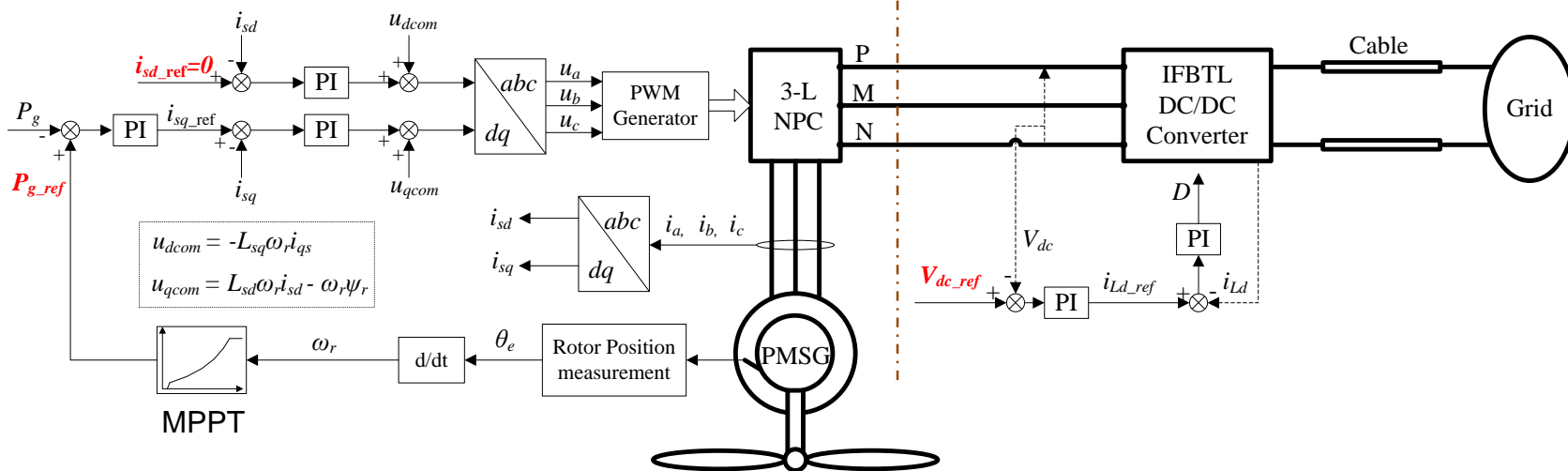


Control Performance

1. 1st-situation

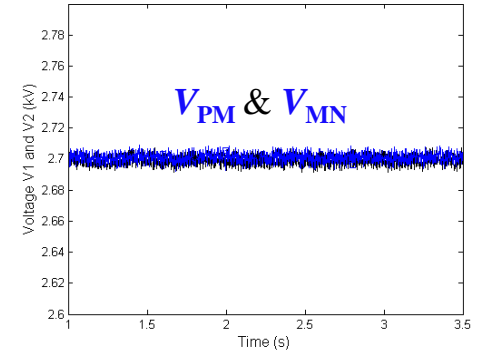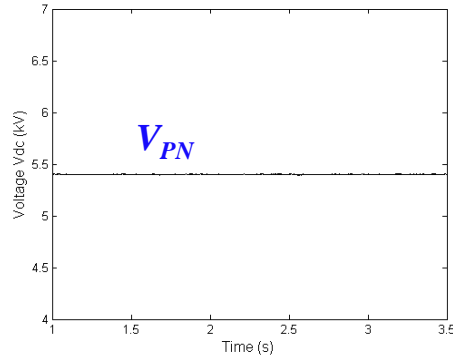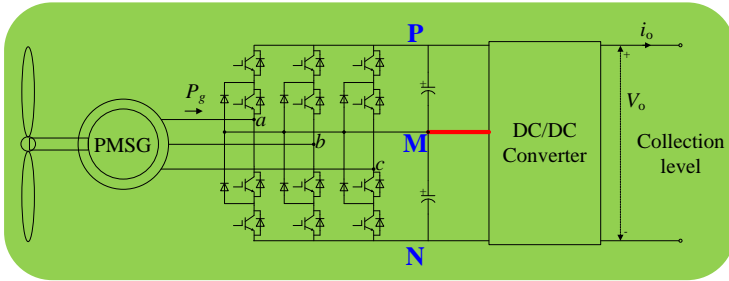

2. 2nd-situation

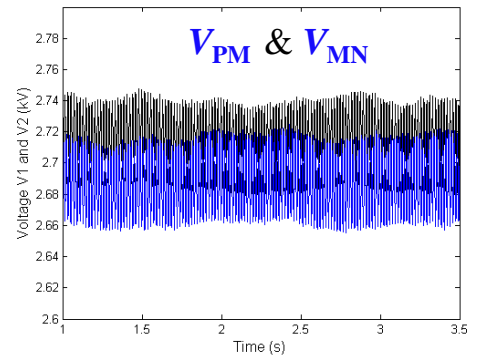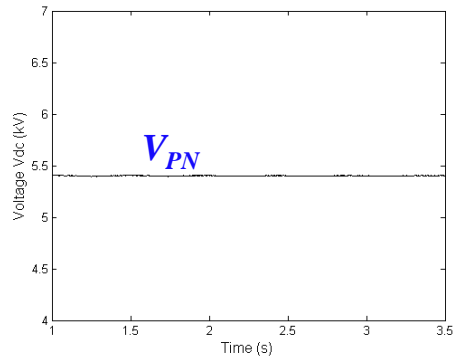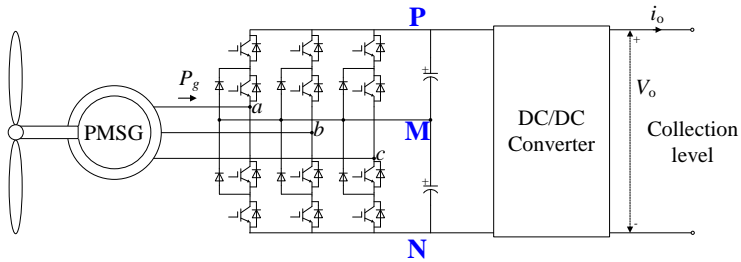


Wind Turbine Control 2






2. Control of wind turbine II

(1) Generator-side converter control

- Optimal power control P_{ref}

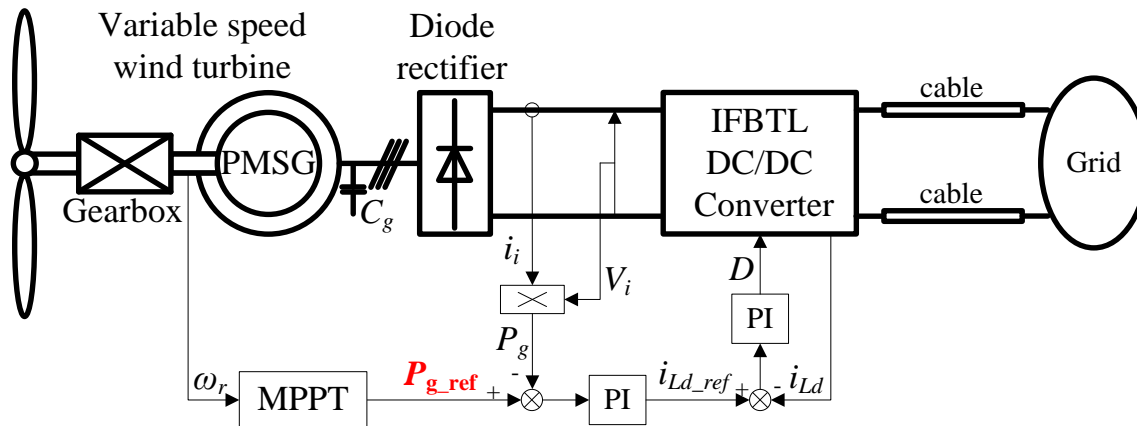


Experiment Test

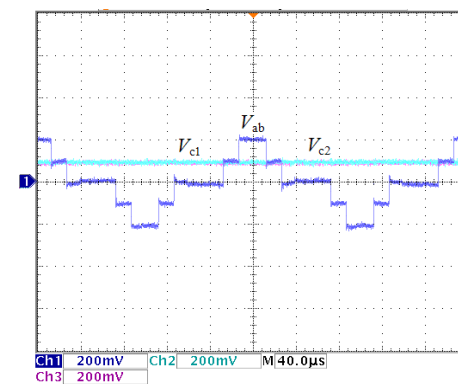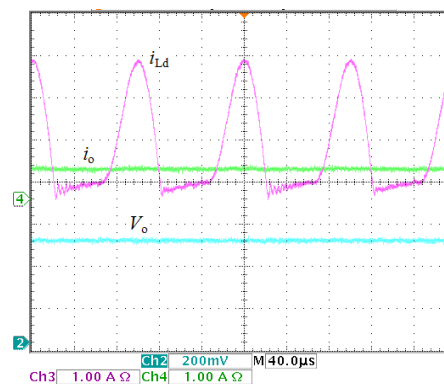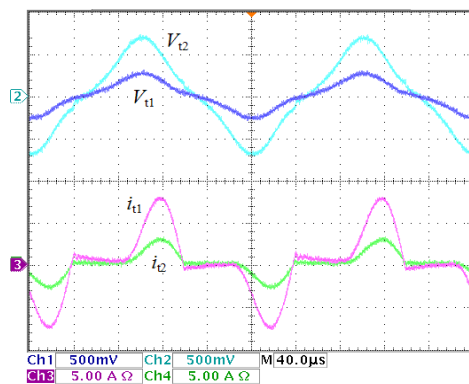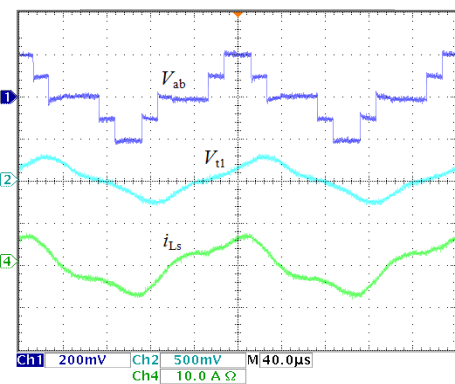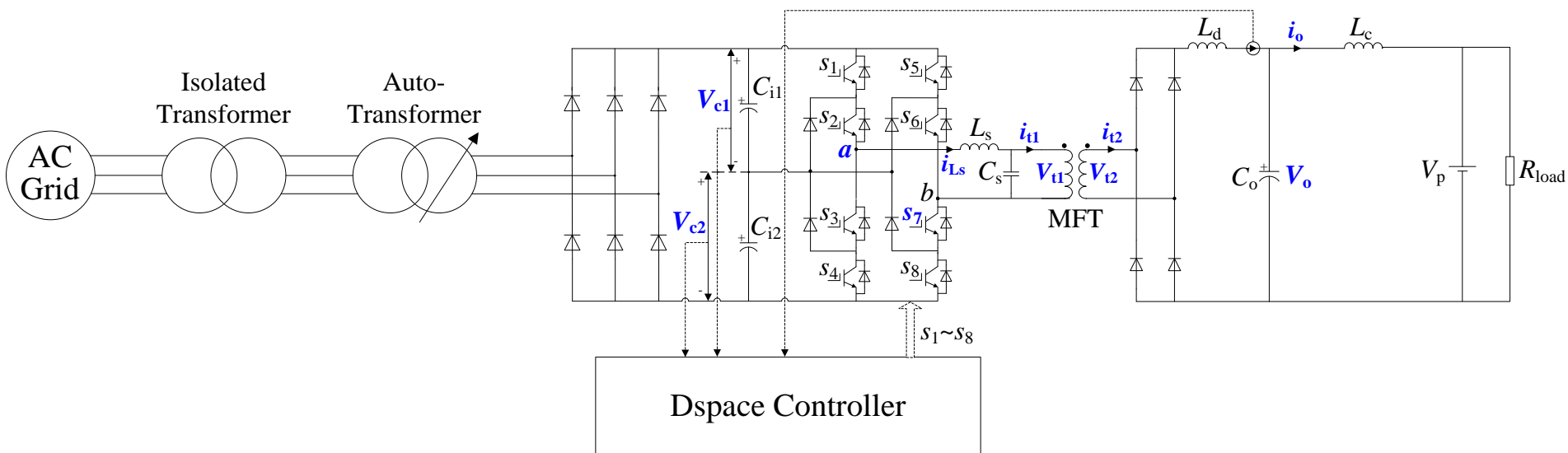


Dynamic Response

1. Current step up


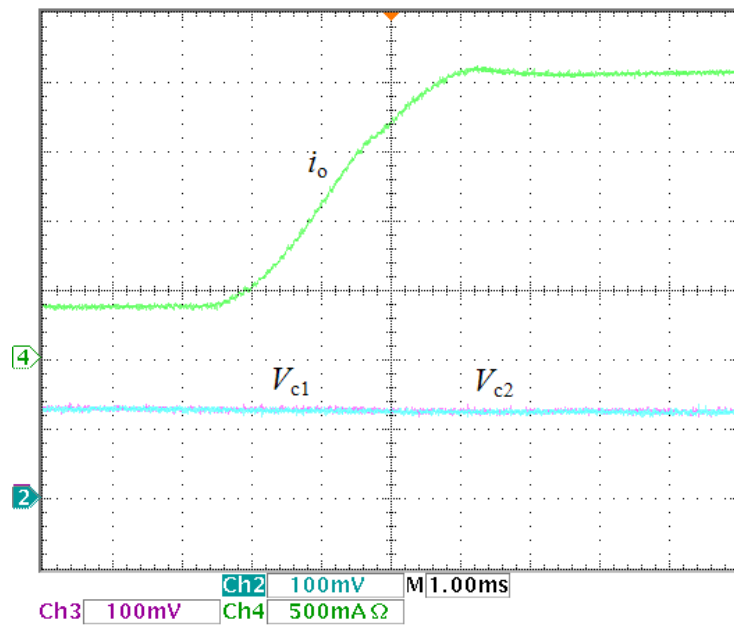


2. Current step down


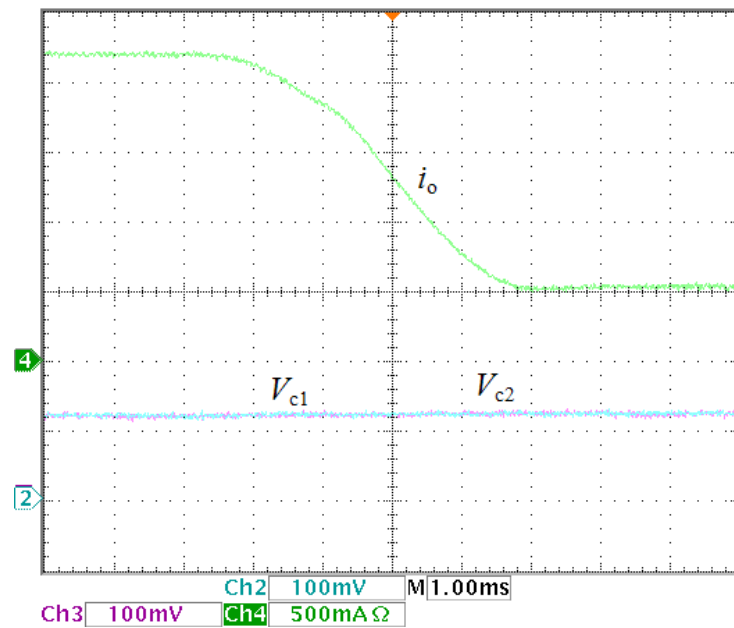


3.4 Wind Turbine for DC Grid

❖ WT Configure 1: 1 stage

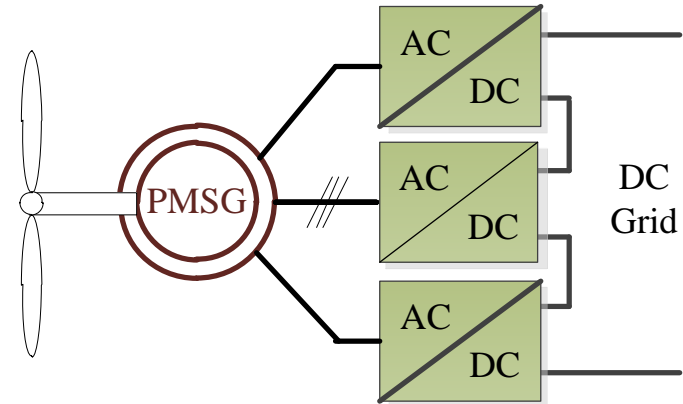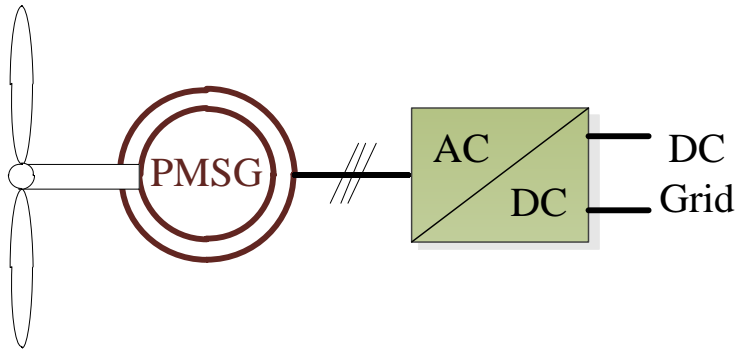


❖ WT Configure 2: 2 stages

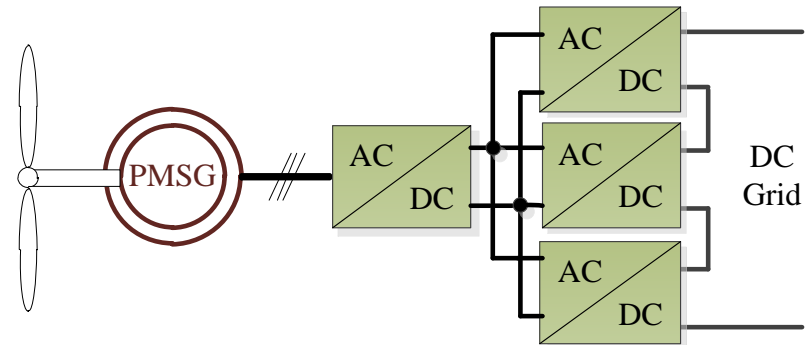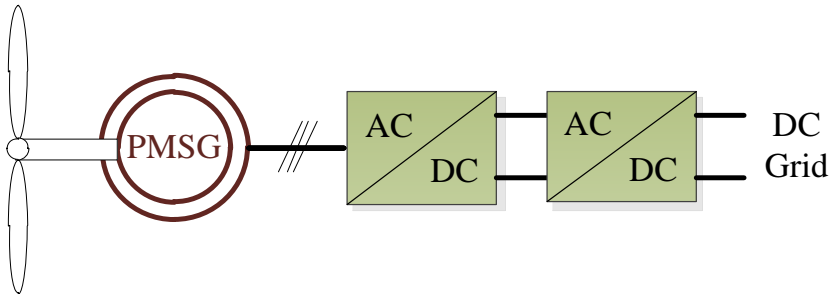

3.5 DC Wind Farm

❖ Configuration 1

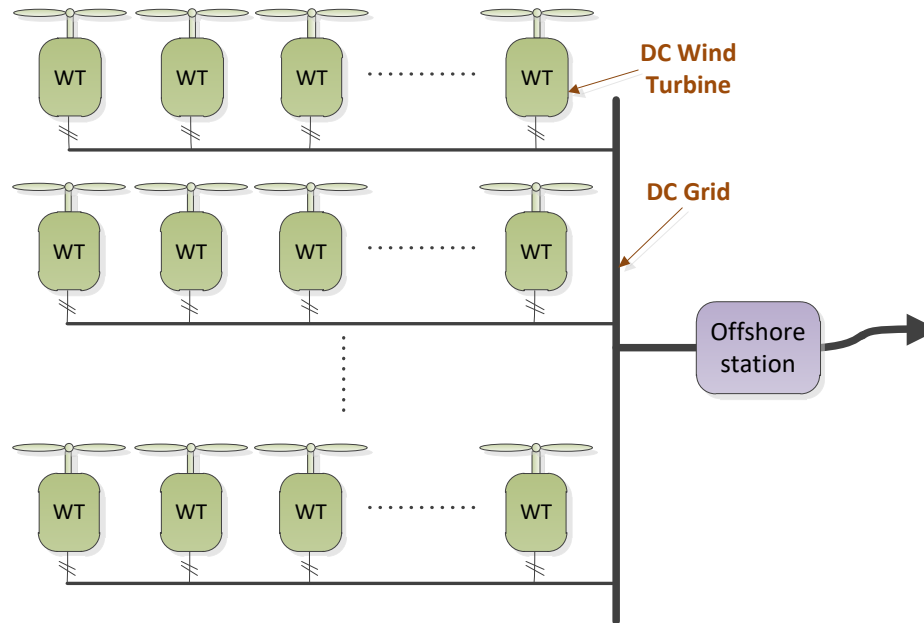


Characteristics:

- ✓ Similar to AC collection system

3.5 DC Wind Farm

❖ Configuration 2

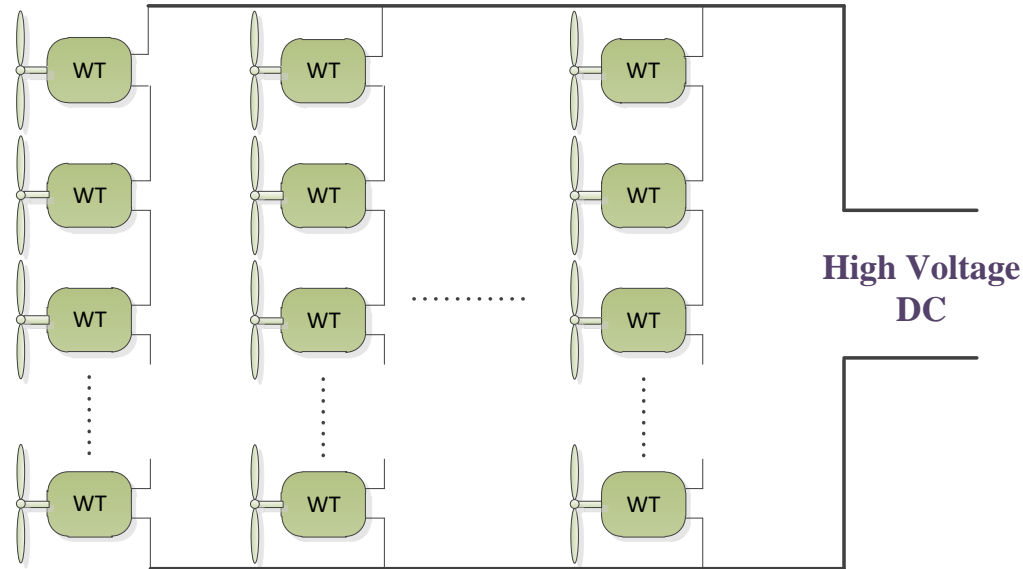

Characteristics:

- ✓ Avoid offshore station
- ✓ Low cost
- ✓ Wind turbines are connected in series
- ✓ Avoid overvoltage of some wind turbine
- ✓ Effect between wind turbines in one cluster
- ✓ Effect among clusters

Conclusions

I. Offshore Wind Farms

- Power converter
- Wind farm configuration

II. DC grid for offshore wind farms

- Power converter
- Wind farm configuration

Thanks !